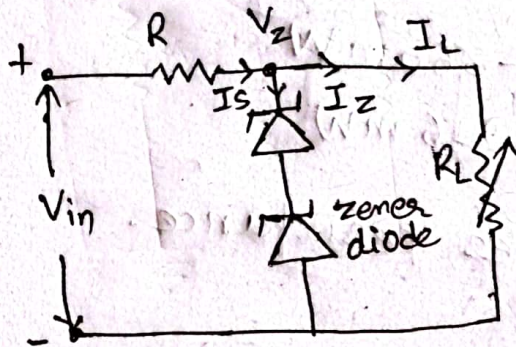


# Diode (Prabin Bhattacharya)

2021- Spring

1. A zener diode regulator consists of two zener diode with 6V zener voltage each, with variable load resistance from  $200\Omega$  to  $1K\Omega$ . Given that below  $V_{in} = 15V$  and  $R = 100\Omega$ .

sol The given zener regulator is:



$$R_{L(\min)} = 200\Omega$$

$$R_{L(\max)} = 1K\Omega = 1000\Omega$$

$$V_{in} = 15V$$


$$R = 100\Omega$$

$$V_Z = V_{Z1} + V_{Z2}$$

$$= 6 + 6$$

$$V_Z = 12V$$

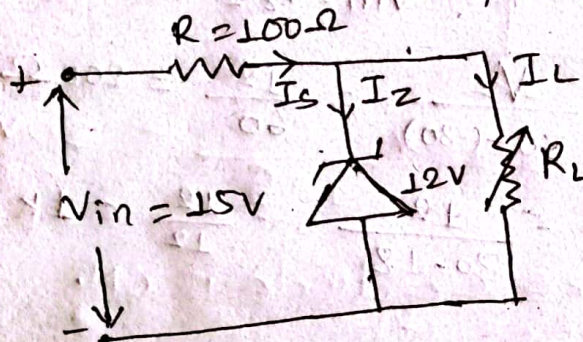The equivalent circuit of zener regulator is



1) Maximum load current,  $I_{L(\max)} = \frac{V_L}{R_{L(\min)}} = \frac{V_Z}{R_{L(\min)}}$

$$= \frac{12}{200} = 60mA$$

And, Minimum load current,  $I_{L(\min)} = \frac{V_L}{R_{L(\max)}} = \frac{V_Z}{R_{L(\max)}}$

$$= \frac{12}{1000} = 12mA$$



$$ii) P_z(\min) = V_z \cdot I_z(\min)$$

$$\text{And } P_z(\max) = V_z \cdot I_z(\max)$$

Now,

$$I = \frac{V_{in} - V_z}{R_s} = \frac{15 - 12}{100} = 30 \text{ mA}$$

$$I_z(\min) = I - I_L(\max) = 30 - 60 = -30 \text{ mA}$$

$$I_z(\max) = I - I_L(\min) = 30 - 12 = 18 \text{ mA}$$

$$\therefore P_z(\min) = 12 \times (-30) = -360 \text{ mW}$$

$$\therefore P_z(\max) = 12 \times (18) = 216 \text{ mW}$$

iii) Voltage drop across series resistance,

$$V_R = I \cdot R_s$$

$$= 30 \times 100$$

$$= 3000 \times 10^{-3}$$

$$\therefore V_R = 3 \text{ V} \quad (\because V_{in} - V_z = 15 - 12 = 3)$$

$$iv) R_L(\min) = \frac{V_L}{I - I_z(\min)} = \frac{V_z}{30 - (-30)} = \frac{12}{60} = 200 \Omega$$

$$R_L(\max) = \frac{V_z}{I - I_z(\max)} = \frac{12}{30 - 18} = \frac{12}{12} = 1 \text{ k}\Omega$$



1. a. If the reverse saturation current of diode is  $5 \text{ nA}$  at  $35^\circ\text{C}$ . find the reverse saturation current at  $235^\circ\text{C}$ .

sol<sup>n</sup> let  $T_1$  and  $T_2$  be the temperature at  $35^\circ\text{C}$  and  $235^\circ\text{C}$  respectively.

i.e.  $T_1 = 35^\circ\text{C}$  &  $T_2 = 235^\circ\text{C}$

Let  $I_1$  and  $I_2$  be the reverse saturation current at  $35^\circ\text{C}$  and  $235^\circ\text{C}$  respectively.

i.e.  $I_1 = 5 \text{ nA}$

$I_2 = ?$

we know that

$$I_2 = \left( 2^{\frac{T_2 - T_1}{10}} \right) \cdot I_1$$

$$= 2^{\frac{235 - 35}{10}} \times 5 \times 10^{-9}$$

$$\therefore I_2 = 5.24 \text{ mA}$$

Thus the reverse saturation current at  $235^\circ\text{C}$  is  $5.24 \text{ mA}$  Ans.

2. For silicon diode, the reverse saturation current is  $20 \mu\text{A}$  at  $27^\circ\text{C}$ . What will be the value of reverse saturation current at  $87^\circ\text{C}$ ?

sol<sup>n</sup> Let  $I_1$  and  $I_2$  be the reverse saturation current at temperature  $T_1 = 27^\circ\text{C}$  and  $T_2 = 87^\circ\text{C}$  respectively.

we know that,  $I_1 = 20 \mu\text{A}$  &  $I_2 = ?$

$$I_2 = \left( 2^{\frac{T_2 - T_1}{10}} \right) \cdot I_1$$

$$= \left( 2^{\frac{87 - 27}{10}} \right) \cdot 20 \times 10^{-6}$$

$$\therefore I_2 = 1.28 \text{ mA}$$


Thus the required value of reverse saturation current at  $87^\circ\text{C}$  is  $1.28 \text{ mA}$ . Ans.




1. For the circuit shown below, find

- i) load voltage,  $V_L$ .
- ii) zener current,  $I_Z$ .
- iii) Power across zener diode,  $P_Z$ .

Sol The given circuit is

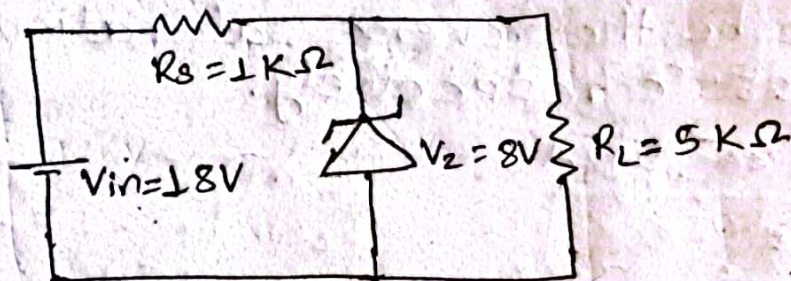


calculating open circuit voltage,

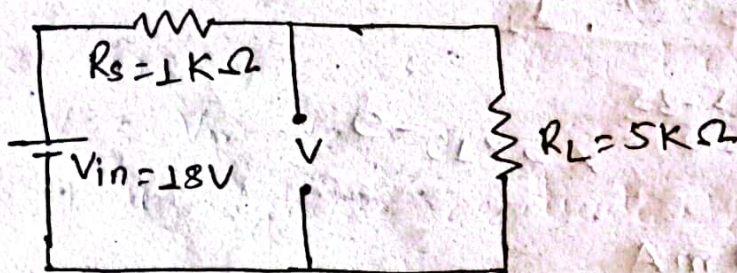

$$\therefore V = V_{in} \times \frac{R_L}{R_s + R_L} = 18 \times \frac{5}{1+5} = 30V$$

Since  $V > V_Z$ , so the zener diode is ON.

The equivalent circuit is

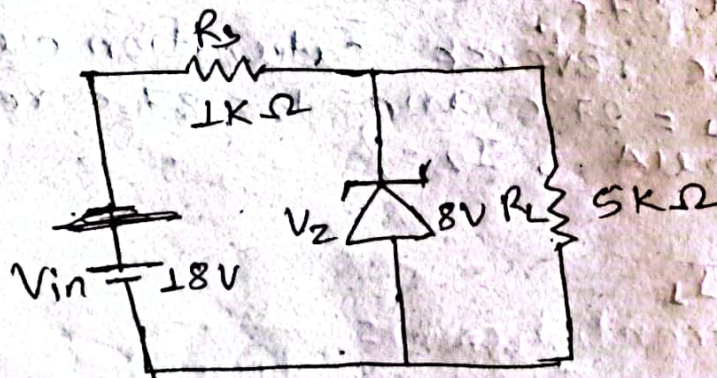

- i) load voltage,  $V_L = \cancel{30} V_Z = 8V$  Ans  
Here, 30



ii) Zener current,  $I_z$   ~~$I_z = 40$~~   
 we know,

$$I = I_L + I_z$$

$$\therefore I_z = I - I_L$$

Now,

$$I_z = I - I_L = \frac{V_{in} - V_z}{R_s} - \frac{V_z}{R_L}$$

$$= \frac{18 - 8}{1000} - \frac{8}{5000} = \frac{10 \times 5 - 8}{5000}$$

$$\therefore I_z = 8.4 \text{ mA} \quad \underline{\text{Ans}}$$

iii) Power across zener diode,  $P_z$ :

$$P_z = V_z \cdot I_z$$

$$= 8 \times 8.4$$

$$\therefore P_z = 67.2 \text{ mW} \quad \underline{\text{Ans}}$$


2. Find the circuit shown in figure, below find

i) Output voltage,  $V_o$


ii) Voltage across series resistance,  $R_s$

iii) Current through zener diode,  $I_z$

so The given circuit is:

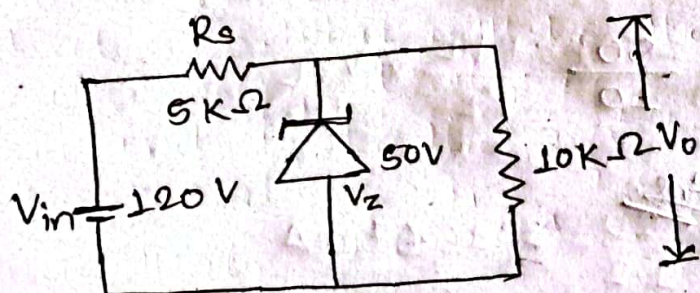

Calculating open circuit voltage,

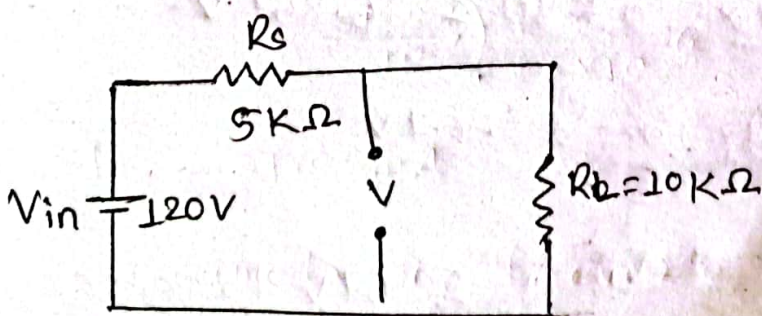




$$\therefore V = V_{in} \times \frac{R_L}{R_s + R_L} = 120 \times \frac{10}{10+5} = 80V$$

Since  $V > V_Z$ , so the zener diode is ON.

The equivalent circuit is

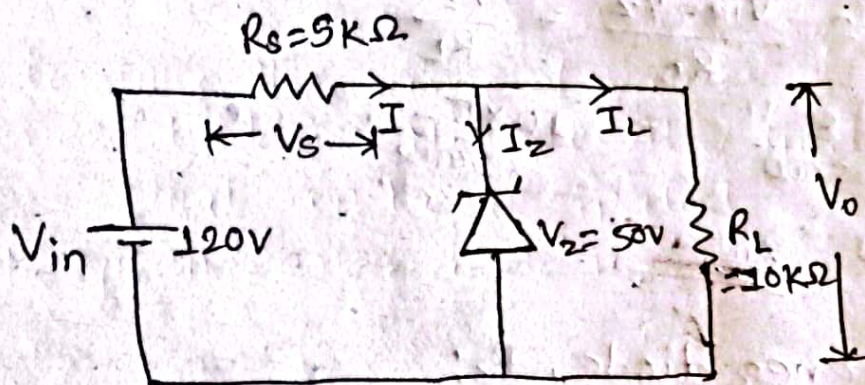

i) Output voltage,  $V_o = V_Z = 50V$  Ans

ii) voltage across series resistance,  $V_s$ :

$$V_s = V_{in} - V_Z = 120 - 50 = 70V \text{ Ans}$$

iii) Current through zener diode,  $I_Z$ :  
we have,

$$I = I_L + I_Z$$

$$\Rightarrow I_Z = I - I_L$$

$$\neq I_Z = \frac{V_{in} - V_Z}{R_s} - \frac{V_Z}{R_L}$$


$$\neq I_Z = \frac{70}{5} - \frac{50}{10}$$

$$\therefore I_Z = 9mA \text{ Ans}$$




3. for the zener diode, network shown in figure, determine  $V_L$ ,  $V_R$ ,  $I_Z$  and  $P_Z$ .

sol The given network is

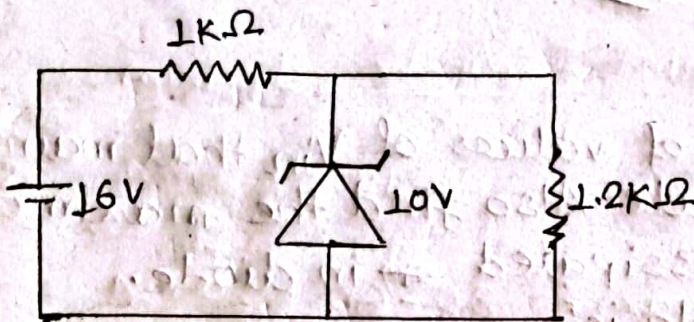


calculating open circuit voltage

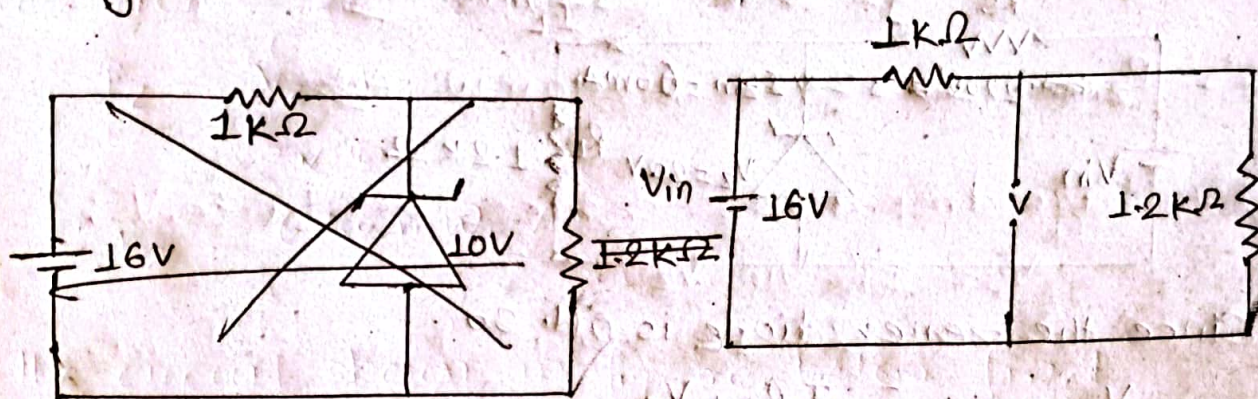

$$\therefore V = \frac{V_{in} \times R_L}{R_S + R_L} = \frac{16 \times 1.2}{1 + 1.2} = 16 \times \frac{1.2}{1 + 1.2}$$

$$= 8.72V$$

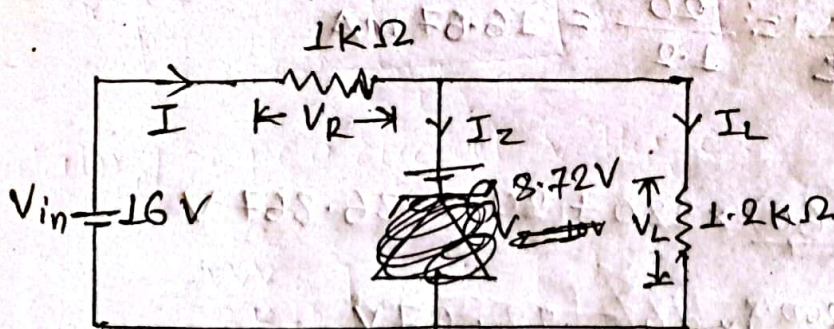Since  $V < V_Z$ , so the zener diode is OFF.  
Now, The equivalent circuit is:



i)  $V_L = V_Z = 10V$  Ans




$$ii) V_R = V_{in} - V_Z = 16.87 - 8.59 = 8.28 \text{ V} \quad \underline{\text{Ans}}$$

$$iii) I_Z = 0 \text{ A} \quad \underline{\text{Ans}}$$

$$iv) P_Z = V_Z \cdot I_Z = 0 \text{ W} \quad \underline{\text{Ans}}$$

4. Determine the range of values of  $V_{in}$  that maintain zener diode is ON state. Also find the maximum power that can be dissipated in diode.

∴ The given zener diode is;

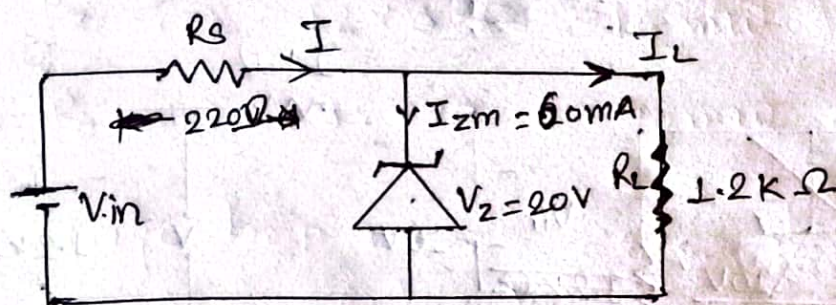

Since the zener diode is ON, so

$$V_{in(max)} = I R_s + V_Z$$

$$\therefore V_{in(max)} = (I_L + I_{Zm}) R_s + 20 \quad (1)$$

Also,

$$V_Z = V_{in(min)} \times \frac{R_L}{R_s + R_L}$$

$$\therefore V_{in(min)} = \frac{R_s + R_L}{R_L} \times V_Z \quad (2)$$

we have,

$$I_L = \frac{V_Z}{R_L} = \frac{20}{1.2} = 16.67 \text{ mA}$$

from (1),

$$V_{in(max)} = \frac{(16.67 + 60)}{1000} \times 220 + 20 = 36.867 \text{ V}$$

$$V_{in(min)} = \left( \frac{220 + 1200}{1200} \right) \times 20 = 23.67 \text{ V}$$

Hence, the range of values of  $V_{in}$  is 23.67 V to 36.867 V, Ans




Maximum power dissipated in zener diode is:

$$\begin{aligned} P_{Zmax} &= V_Z \cdot I_{Zm} \\ &= 20 \times 60 \\ &= 1.2 \text{ W} \quad \underline{\underline{Ans}} \end{aligned}$$

5. A zener regulator has 12V zener voltage with variable load resistance. Calculate

- Maximum and minimum load current
- Maximum and minimum power dissipated across load.
- Voltage drop across series resistance
- Maximum value of load resistance to ensure that zener diode is ON.

Q The given zener diode circuit is:-

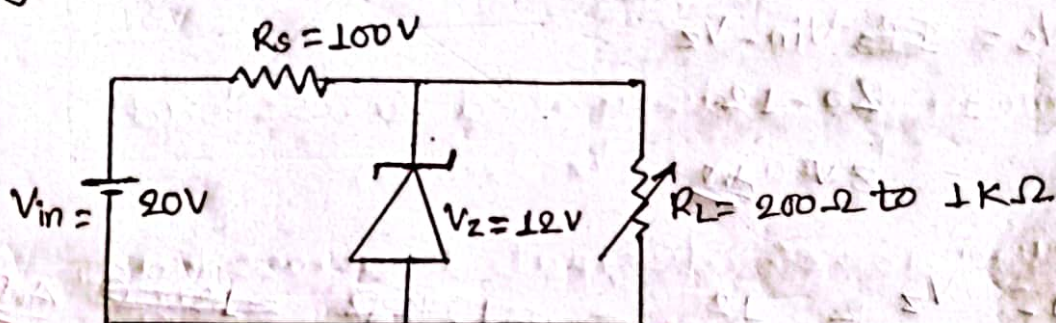

Calculating

Since the zener diode is ON.

$$V_{in} = 20 \text{ V}$$

$$R_s = 100 \Omega$$

$$V_Z = 12 \text{ V}$$

$$R_{L(\min)} = 200 \Omega$$

$$R_{L(\max)} = 1 \text{ K}\Omega = 1000 \Omega$$

i) Maximum load current,  $I_{L(\max)}$ :

$$\text{we know, } I_{L(\max)} = \frac{V_L}{R_{L(\min)}} = \frac{V_Z}{R_{L(\min)}} = \frac{12}{200} = 60 \text{ mA}$$

And,

$$\text{Minimum load current, } I_{L(\min)} = \frac{V_Z}{R_{L(\max)}} = \frac{12}{1000} = 12 \text{ mA}$$



ii) Maximum power dissipated across load,

$$P_{Z(max)} = V_Z \cdot I_{Z(max)}$$

$$P_{Z(min)} = V_Z \cdot I_{Z(min)}$$

Now,

$$I_{Z(max)} = I - I_{L(min)} = \frac{V_{in} - V_Z}{R_s} - I_{L(min)}$$

$$\therefore I_{Z(max)} = \frac{20 - 12}{100} - 12 = 80 - 12 = 68 \text{ mA} \quad \text{Ans}$$

$$\text{Also, } I_{Z(min)} = I - I_{L(max)} = 80 - 60 = 20 \text{ mA}$$

Now,

$$\therefore P_{Z(max)} = 12 \times 68 = 816 \text{ mW} \quad \text{Ans}$$

$$\therefore P_{Z(min)} = 12 \times 20 = 240 \text{ mW} \quad \text{Ans}$$

iii) Voltage drop across series resistance,  $V_s$ :

$$V_s = V_{in} - V_Z$$


$$= 20 - 12$$

$$= 8 \text{ V} \quad \text{Ans}$$

$$iv) R_{L(max)} = \frac{V_Z}{I - I_{Zm}} = \frac{12}{80 \text{ mA} - 68 \text{ mA}} = 1 \text{ k}\Omega \quad \text{Ans}$$

6. For the given circuit, load current varies from 12 mA to 100 mA. Find the value of series resistance  $R_s$  to maintain 7.2 V across the load. Maximum zener diode current is 10 mA.

sol The given circuit is:

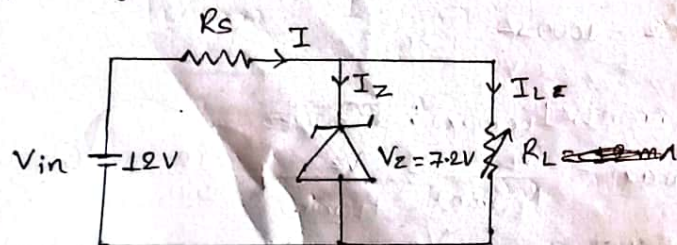

Given:

$$V_{in} = 12 \text{ V}$$

$$V_Z = 7.2 \text{ V}$$

$$I_{L(min)} = 12 \text{ mA}$$

$$I_{L(max)} = 100 \text{ mA}$$

$$I_{Z(min)} = 10 \text{ mA}$$

$$\therefore I = I_{L(max)} + I_{Z(min)}$$

$$= 100 + 10$$

$$\therefore I = 110 \text{ mA}$$


Now,

$$\text{Series resistance, } R_s = \frac{V_{in} - V_Z}{I} = \frac{12 - 7.2}{110}$$

$$= 43.63 \Omega \quad \text{Ans}$$

7. For the circuit given, find the maximum and minimum value of load resistor  $R_L$  required for safe turn 'ON' of zener diode. Also find the minimum and maximum power that can be dissipated across load.

sol The given circuit is:

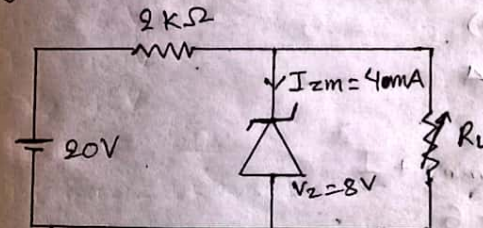

Given:

$$V_{in} = 20 \text{ V}$$

$$R_s = 2 \text{ k}\Omega$$

$$V_Z = 8 \text{ V}$$

$$I_{Zm} = 40 \text{ mA}$$



we know,

$$I = \frac{V_{in} - V_z}{R_s} = \frac{20 - 8}{2 \times 1000} = 6 \text{ mA}$$

i) Maximum load resistor,  $R_{L(\max)} = \frac{V_z}{I - I_{z(\max)}}$

$$= \frac{8}{6 - 4}$$
$$\therefore R_{L(\max)} = 4 \text{ k}\Omega \text{ Ans}$$

Also,

Minimum load resistor,  $R_{L(\min)} = \frac{V_z}{I}$

$$= \frac{8}{6}$$
$$\therefore R_{L(\min)} = 1.33 \text{ k}\Omega \text{ Ans}$$

ii) Maximum power dissipated across load,  
 $P_{z(\max)} = V_z \cdot I_{z(\max)}$

Minimum power dissipated across load,  
 $P_{z(\min)} = V_z \cdot I_{z(\min)}$

Now,  $I = I_{z(\max)} + I_{L(\min)}$

$$\Rightarrow 6 = 4 + I_{L(\min)}$$

$$\therefore I_{L(\min)} = 2 \text{ mA}$$

Also,

$$I_{L(\max)} = I_{z(\min)} + I$$
$$= 0 + 6$$

$$\therefore I_{L(\max)} = 6 \text{ mA}$$

we have


$$\therefore P_{z(\max)} = 8 \times 6 = 48 \text{ mW Ans}$$

$$\therefore P_{z(\min)} = 8 \times 0 = 0 \text{ mW Ans}$$

2021-Fall

1. b. What value of series resistance ( $R$ ) is required when three  $10 \text{ W}$ ,  $10 \text{ V}$ ,  $1000 \text{ mA}$  zener diodes are connected in series to obtain a  $30 \text{ V}$  regulated output from a  $45 \text{ V}$  dc power source?

soln The given circuit is:-

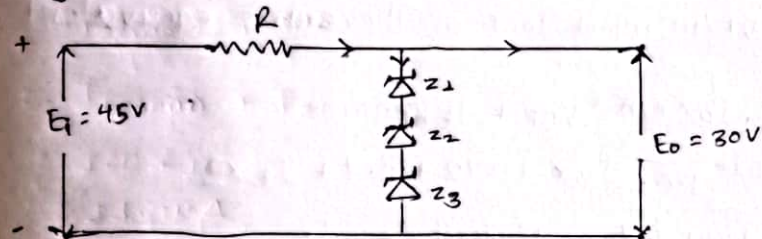


$$\therefore V_z = V_{Z1} + V_{Z2} + V_{Z3}$$
$$= 10 + 10 + 10$$
$$\therefore V_z = 30 \text{ V}$$

$$\therefore P_z = 10 + 10 + 10$$
$$= 30 \text{ W}$$

$$\therefore I_z = 1000 \text{ mA} = 1 \text{ A}$$

The equivalent circuit is:

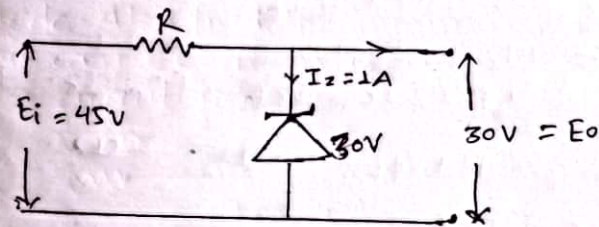

$$\therefore V_R = 45 - 30 = 15 \text{ V}$$

$$\therefore R = \frac{V_R}{I} = \frac{15}{I_z + I_L} = \frac{15}{1 + 0} = 15 \Omega$$

we know,


$$V_z = V_o$$
$$\Rightarrow 30 = I_L R_L$$



## BJT (Prabin Chaudhary)

2.6 In the given silicon-biased circuit  $\beta = 100$ , draw the DC and AC load line and determine the operating point.

The given circuit is:

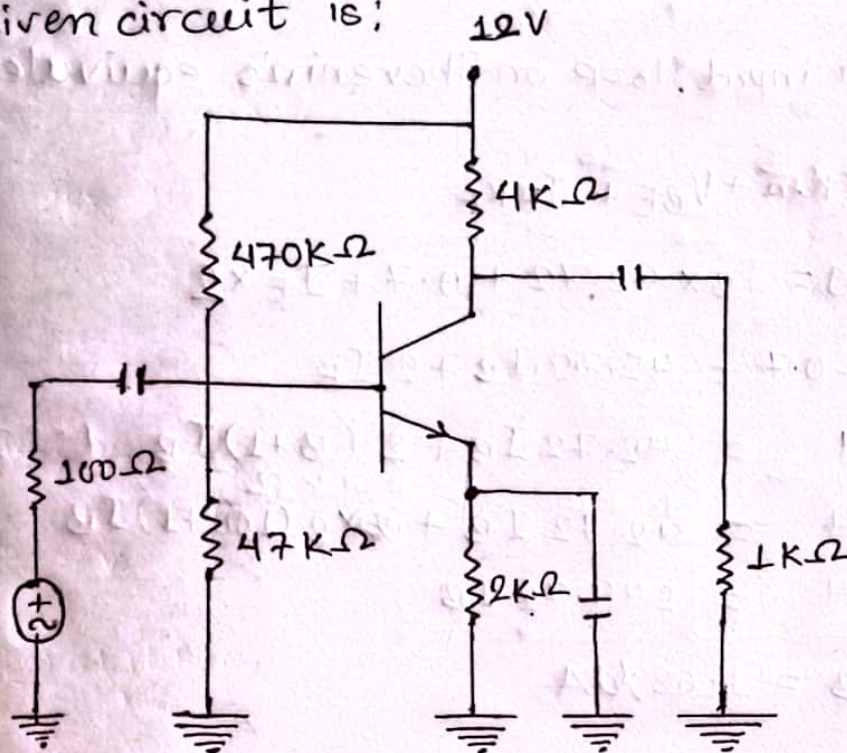

The dc equivalent circuit and Thevenin's equivalent circuit are:

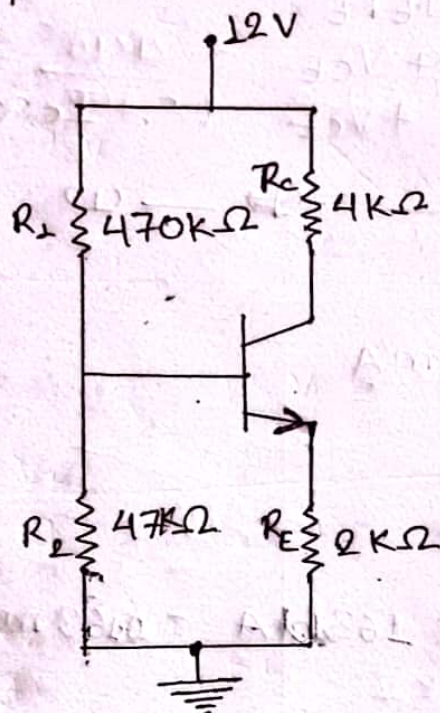


fig. dc equivalent circuit

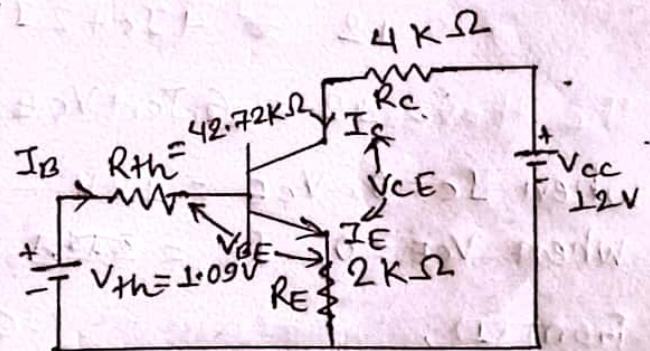


fig. Thevenin's equivalent circuit



Here,

$$R_{th} = R_1 // R_2 = \frac{470 \times 47}{470 + 47} = 42.72 \text{ k}\Omega$$

$$V_{th} = V_{cc} \times \frac{R_2}{R_1 + R_2} = 12 \times \frac{47}{470 + 47} = 1.09 \text{ V}$$

Applying KVL in input loop on Thevenin's equivalent circuit, we get;

$$V_{th} = I_B \times R_{th} + V_{BE} + I_E R_E$$

$$\Rightarrow 1.09 = I_B \times 42.72 + 0.7 + I_E \times 2$$

$$\Rightarrow 1.09 - 0.7 = 42.72 I_B + 2 I_E$$

$$\Rightarrow 0.4 = 42.72 I_B + 2 (\beta + 1) I_B \quad (\because I_E = (\beta + 1) I_B)$$

$$\Rightarrow 0.4 = 42.72 I_B + 2 (100 + 1) I_B$$

$$\Rightarrow 0.4 = 244.72 I_B$$

$$\therefore I_B = 1.63 \text{ }\mu\text{A}$$

Applying KVL in output loop, we get on Thevenin's equivalent circuit, we get;

$$V_{cc} = 4 I_C + V_{CE} + I_E R_E$$

$$\Rightarrow 12 = 4 I_C + 2 I_E + V_{CE}$$

$$\Rightarrow 12 = 4 I_C + 2 I_C + V_{CE} \quad (\because I_C \approx I_E)$$

$$\therefore 12 = 6 I_C + V_{CE} \quad \text{--- (1)}$$

When  $I_C = 0$ ,  $V_{CE} = 12 \text{ V}$

When  $V_{CE} = 0$ ;  $I_C = 2 \text{ mA}$

From (1),

$$12 = 6 I_{CQ} + 12$$

We know,

$$I_{CQ} = \beta I_B = 100 \times 1.63 = 163 \text{ }\mu\text{A} = 0.163 \text{ mA}$$

$\therefore$  From (1),




$$12 = 6 \times 0.163 + V_{CE}$$

$$\Rightarrow 12 - 0.978 = V_{CE}$$

$$11.022 \text{ V}$$

$$\therefore V_{CEQ} = 11.022 \text{ V}$$

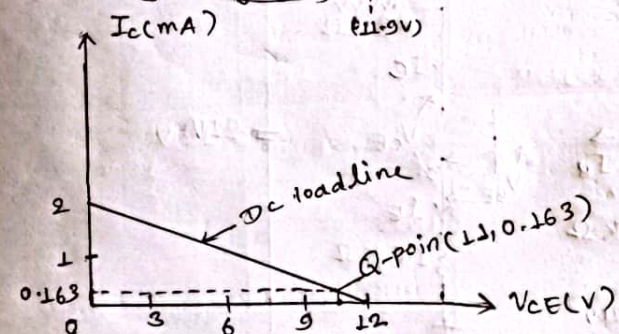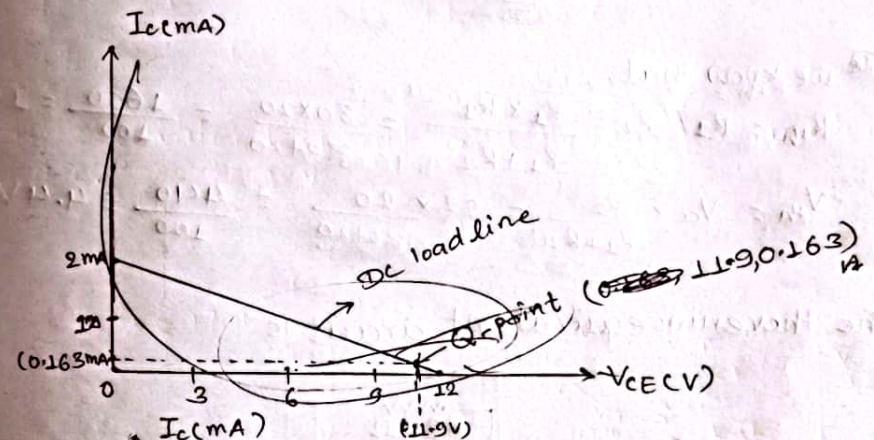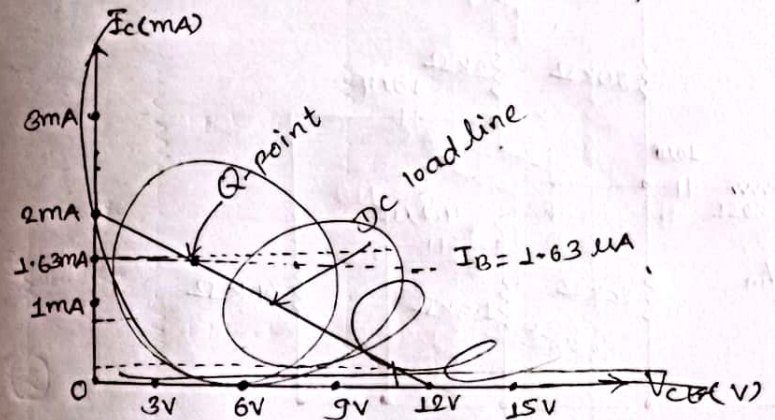
The dc load line is the straight line joining two points (12, 0) and (2 mA, 0) as shown in the output characteristics of CE transistor configuration.





2b. For the BJT common emitter circuit shown below, determine the operating point and locate it in the load line. Assume  $\beta = 100$ .

sol The given CE circuit is;

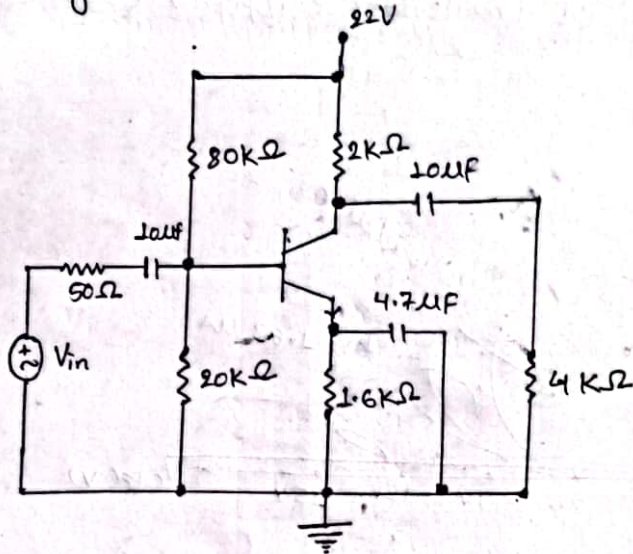


we know that,

$$R_{Th} = R_1 // R_2 = \frac{R_1 \times R_2}{R_1 + R_2} = \frac{80 \times 20}{80 + 20} = \frac{1600}{100} = 16k\Omega$$

$$V_{Th} = V_{CC} \times \frac{R_2}{R_1 + R_2} = 22 \times \frac{20}{80 + 20} = \frac{440}{100} = 4.4V$$

The thevenin's equivalent circuit is

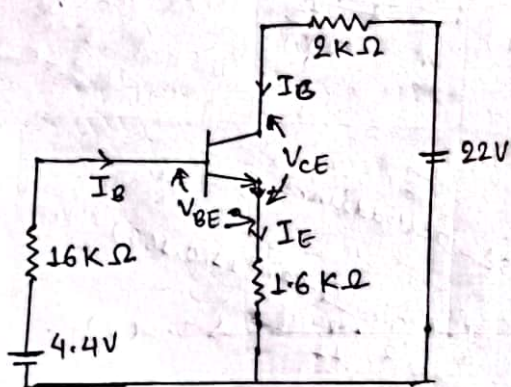

Applying KVL in input loop, we get:-

$$4.4 = 16 \times I_B + V_{BE} + 1.6 \times I_E$$

$$\Rightarrow 4.4 = 16 I_B + 0.7 + 1.6 \times (100 + 1) I_B$$

$$\Rightarrow 4.4 - 0.7 = 177.6 I_B$$

$$\Rightarrow \frac{3.7}{177.6 \times 1000} = I_B$$

$$\therefore I_B = 20.8 \mu A$$

Applying KVL in output loop, we get:-

$$22 = 2 \times I_C + V_{CE} + 1.6 \times I_E$$

$$\Rightarrow 22 = 2 I_C + 1.6 I_C + V_{CE} \quad (\because I_C \approx I_E)$$

$$\Rightarrow 22 = 3.6 I_C + V_{CE} \quad \text{--- (1)}$$

when  $I_C = 0$ ,  $V_{CE} = 22$

when  $V_{CE} = 0$ ,  $I_C = 13.75 \text{ mA}$

we know,

$$I_{CQ} = \beta I_B = 100 \times 20.8 \times 10^{-6} = 2.08 \text{ mA}$$

from (1),


$$V_{CEQ} = 22 - 3.6 \times 2.08 \times 10^{-3}$$

$$\therefore I_E = I_C + I_B = 2.08 \times 10^{-3} + 20.8 \times 10^{-6} = 2.1 \text{ mA}$$

from (1),

$$22 - 3.6 \times 2.08 = V_{CEQ}$$

$$\therefore V_{CEQ} = 14.5 \text{ V}$$

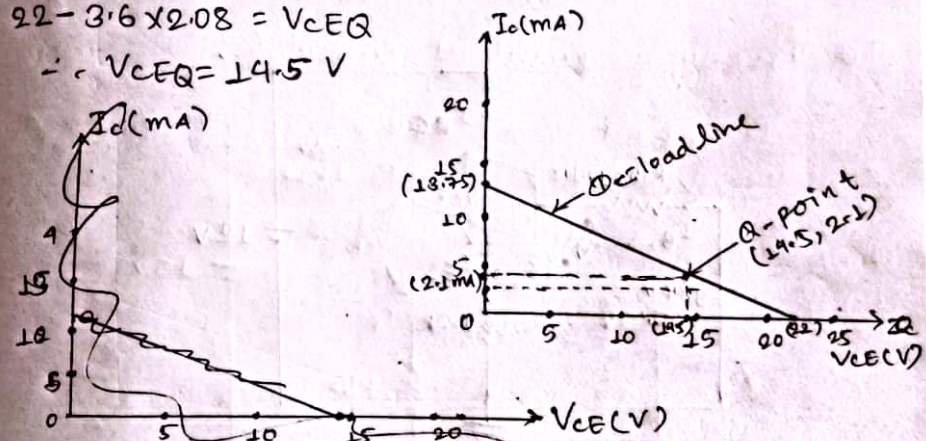




2.b. For the emitter follower network of figure below

i) Find  $I_B$ ,  $I_C$  and  $I_E$

ii) Determine  $V_B$ ,  $V_C$ , and  $V_E$

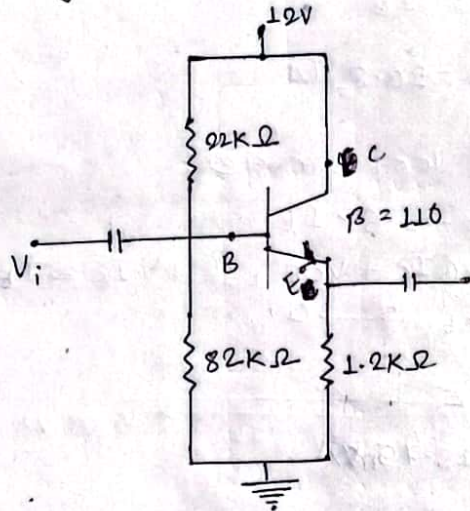iii) calculate  $V_{CE}$


Sol The given emitter follower network is shown below



Now,  $R_{Th} = \frac{22 \times 82}{22 + 82} = 17.34 k\Omega$

$V_{Th} = 12 \times \frac{82}{22 + 82} = 9.46 V$

The Thevenin's equivalent circuit is:

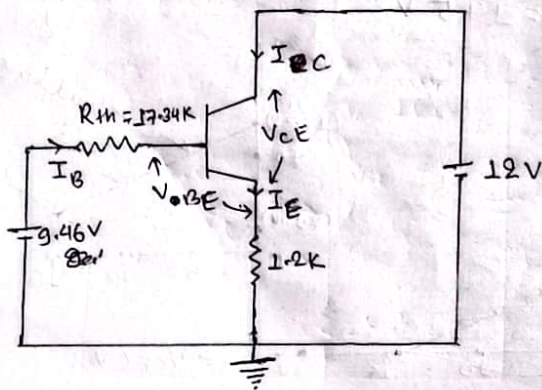

Now Applying KVL in input loop, we get:

$$9.46 = 17.34 I_B + V_{BE} + 1.2 I_E$$

$$\Rightarrow 9.46 = 17.34 I_B + 0.7 + 1.2 (\beta + 1) I_B$$

$$\Rightarrow 9.46 - 0.7 = 17.34 I_B + 1.2 (110 + 1) I_B$$

$$\Rightarrow 8.76 = 150.54 I_B$$

$$\therefore I_B = 0.58 \mu A \text{ Ans.}$$

Also we know,

$$I_C = \beta I_B = 110 \times 0.58 \times 10^{-6} = 0.64 \mu A \text{ Ans.}$$

$$I_E = (\beta + 1) I_B = 111 \times 0.58 \times 10^{-6} = 0.64 \mu A \text{ Ans.}$$

Now,

$$V_B = V_{Th} = 9.46 V \text{ Ans.}$$

$$V_C = I_C R_C = I_C \times 0 = 0 V \text{ Ans.}$$

$$V_E = I_E R_E = 0.64 \times 10^{-6} \times 1.2 \times 10^3 = 0.768 mV \text{ Ans.}$$




2016-Spring

2.c. An NPN silicon transistor having a normal  $\beta$  of 100 is to be used in a CE configuration with  $V_{CC} = 15V$ . The Q-point is to be  $I_C = 4mA$  and  $V_{CE} = 12V$ . Now design the circuit diagram.

Given;

$$\begin{aligned}\beta &= 100 \\ V_{CC} &= 15V \\ I_{CQ} &= 4mA \\ V_{CEQ} &= 12V\end{aligned}$$

The required circuit diagram will be

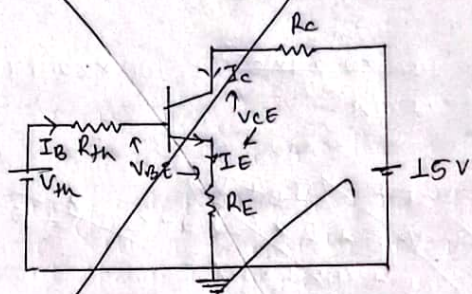

Apply KVL in output loop, we get;  
 $15 = I_C R_C + V_{CE} + I_E R_E$

We have,

$$\begin{aligned}I_C &= \beta I_B \\ \Rightarrow I_B &= \frac{I_C}{\beta} = \frac{4 \times 10^{-3}}{100} = 0.04mA\end{aligned}$$

$$\therefore I_E = (\beta + 1) I_B = 101 \times 0.04 \times 10^{-3} = 4.04mA$$

Assuming,  $V_T = 26mV$

$$\beta_m = \frac{I_C}{V_T} = \frac{4}{26} = 0.153$$

Since  $V_{CC} \geq 15$ , so we use guideline 2 ( $1/10^{th}$  rule) for the design of bias circuit.  
From ( $1/10^{th}$ ) rule,

$$V_E = I_E R_E = \frac{V_{CC}}{10}$$

$$\Rightarrow 4.04 R_E = \frac{15}{10} = 1.5$$

$$\therefore R_E = \frac{1.5}{4.04 \times 10^{-3}} = 371.28 \Omega = 0.371K\Omega$$

Also,

$$V_{RC} = \frac{4}{10} V_{CC} = \frac{4}{10} \times 15 = 6$$

$$\Rightarrow I_C R_C = 6$$

$$\Rightarrow R_C = \frac{6}{4 \times 10^{-3}} = 1500 = 1.5K\Omega$$

Using stiff voltage divider biasing,

$$R_2 = 0.01 \beta R_E = 0.01 \times 100 \times 0.371 \times 10^3$$

$$\therefore R_2 = 0.371K\Omega$$

For stiff biasing,

$$I_{R12} = I_E = 4.04mA$$

where,  $I_{R12}$  is the series current flowing through  $R_1$  and  $R_2$ .

The application of KVL results,

$$V_{CC} = I_{R12} (R_1 + R_2)$$

$$\Rightarrow 15 = 4.04 \times 10^{-3} (0.371 + R_1)$$


$$\Rightarrow \frac{15}{4.04 \times 10^{-3}} = 0.371 + R_1$$

$$\Rightarrow R_1 = \frac{15}{4.04 \times 10^{-3}} - 0.371 \times 1000$$

$$\therefore R_1 = 3.34K\Omega$$



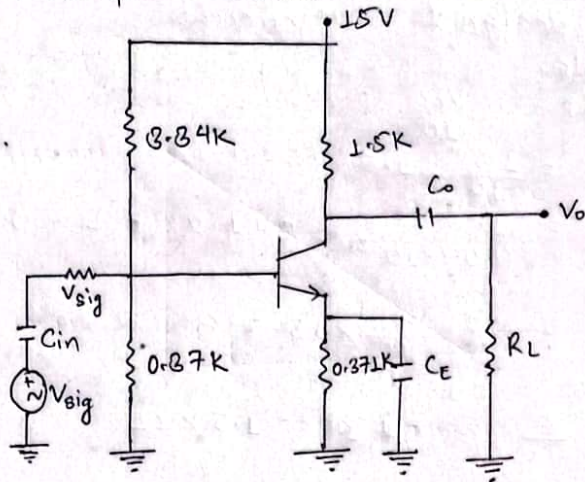
Thus the complete common emitter circuit is:



21b.

(2015-Spring)

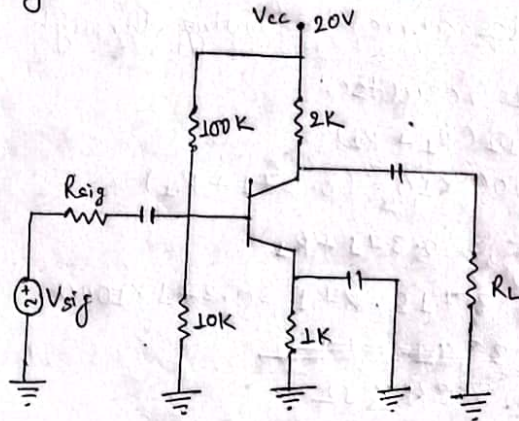For the circuits shown below, draw the dc load line and find the operating point. Also find the stability  $S$  of the circuit. (Assume silicon transistor  $\beta = 100$ ).  
 The given circuit shown below is:




We know that

$$R_{Th} = \frac{10 \times 100}{10 + 100} = 9.1 \text{ K}\Omega$$

$$V_{Th} = V_{cc} \times \frac{10}{10 + 100} = \frac{20 \times 10}{110} = 1.8 \text{ V}$$

The Thevenin's equivalent circuit is:

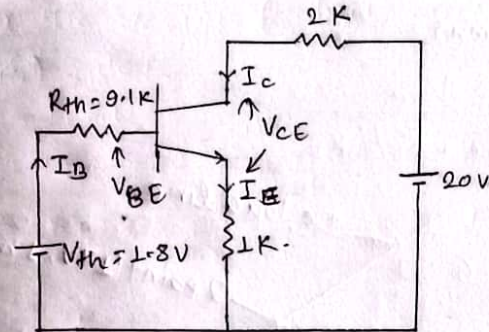

Applying KVL in input loop, we get:

$$1.8 = 9.1 I_B + V_{BE} + I_E$$

$$\Rightarrow 1.8 = 9.1 I_B + 0.7 + 10 I_B$$

$$\Rightarrow 1.8 - 0.7 = 19.1 I_B$$

$$\therefore I_B = 9.99 \approx 10 \mu\text{A}$$

Applying KCL in output loop, we get:

$$20 = 2 I_C + V_{CE} + I_E$$

$$\Rightarrow 20 = 2 I_C + V_{CE} + I_C \quad (\because I_C \approx I_E)$$

$$\Rightarrow 20 = 3 I_C + V_{CE} \quad (1)$$

when  $I_C = 0$ ,  $V_{CE} = 20 \text{ V}$


when  $V_{CE} = 0$ ,  $I_C = 6.67 \text{ mA}$

We know,


$$I_{CQ} = \beta I_B = 100 \times 10 \times 10^{-6} = 1 \text{ mA}$$

$$V_{CEQ} = 20 - 3 \times 1 = 17 \text{ V}$$

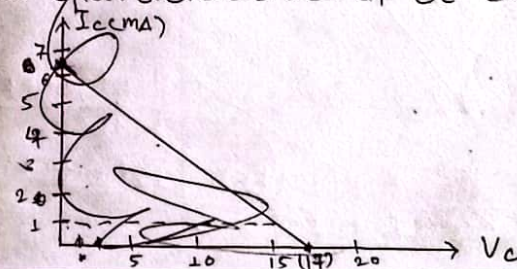The dc load line and operating point is shown in output characteristics of CE configuration.






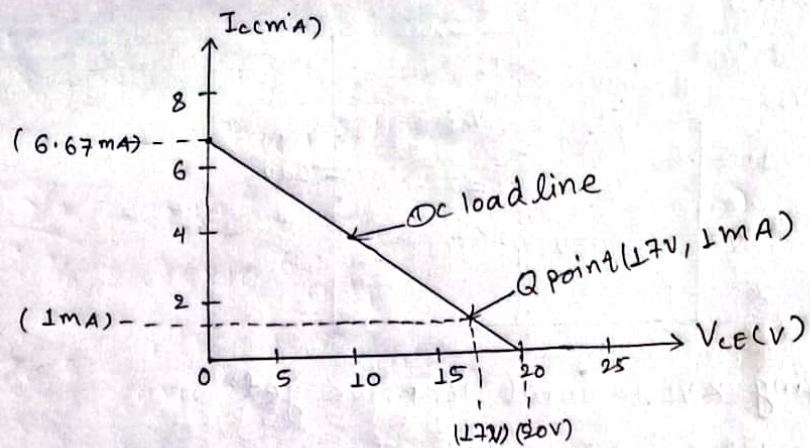


## Small signal frequency model (Prabin)

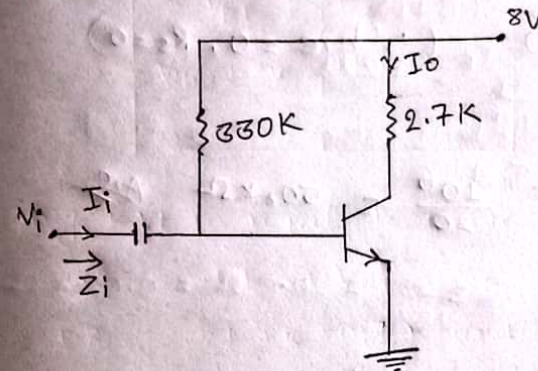4. b. Find  $A_{vs}$ ,  $A_v$ ,  $Z_o$ ,  $Z_{in}$  of the following circuit diagram - using h-parameter. (Given:  $h_{fe} = 100$ ,  $h_{ie} = 1.175 \text{ K}$ ,  $h_{oe} = 20 \mu\text{A/V}$ )  
 The given circuit diagram is



The h-model of given circuit diagram is:

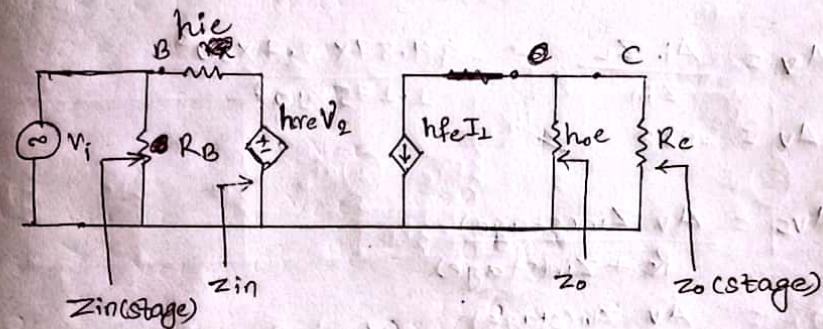

Here,

$$Z_L = R_C = 2.7 \text{ K}\Omega$$

$$R_B = 330 \text{ K}\Omega$$

$$\begin{aligned} i) Z_{in} &= h_{ie} - \frac{h_{fe} h_{re}}{h_{oe} + Y_L} = 1.175 \text{ K}\Omega - 0 \quad (\because h_{re} = 0) \\ &= 1.175 \text{ K}\Omega \quad \text{Ans} \end{aligned}$$



$$ii) Z_o = \frac{1}{Y_o}$$

we know,

$$Y_o = h_{oe} - \frac{h_{fe} h_{re}}{h_{ie} + R_s // R_B}$$

$$\Rightarrow Y_o = 20 \times 10^{-6} - 0 \quad (\because h_{re} = 0, R_s = 0)$$

$$\therefore Y_o = 20 \times 10^{-6}$$

$$\text{Now, } Z_o = \frac{1}{20 \times 10^{-6}} = \frac{10^6}{20} = 50 \text{ k}\Omega \quad \text{Ans}$$

$$iii) A_{vi} = \frac{-h_{fe}}{1 + h_{oe} Z_L}$$

$$= \frac{-100}{1 + 20 \times 10^{-6} \times 2.7 \times 10^3}$$

$$\therefore A_{vi} = -94.87 \quad \text{Ans}$$

$$iv) A_v = \frac{A_{vi} Z_L}{Z_{in}} = \frac{-94.87 \times 2.7 \times 10^3}{1.175 \times 10^3}$$

$$\therefore A_v = -218 \quad \text{Ans}$$

$$v) A_{vs} = \frac{A_v Z_{in(stage)}}{R_s + Z_{in(stage)}}$$

$$= \frac{A_v Z_{in(stage)}}{Z_{in(stage)}} \quad (\because R_s = 0)$$

$$\therefore A_{vs} = A_v = -218 \quad \text{Ans}$$

2017-Spring


Q. b) For the given CE amplifier, find the following using re model

i. input impedance

ii. output impedance

iii. voltage gain (Assume  $\beta = 90$ ,  $V_{cc} = +19V$ )

The given CE amplifier is:-

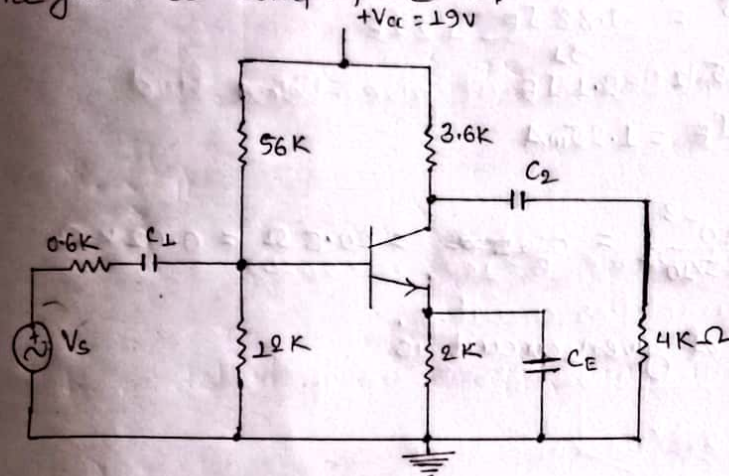

we know,


$$r_e = \frac{26 \text{ mV}}{I_E}$$

We have

$$R_{th} = \frac{56 \times 12}{56 + 12} = 9.88 \text{ k}\Omega$$

$$V_{th} = V_{cc} \times \frac{12}{56 + 12} = \frac{19 \times 12}{56 + 12} = 3.35 \text{ V}$$

The Thevenin's equivalent circuit is:-

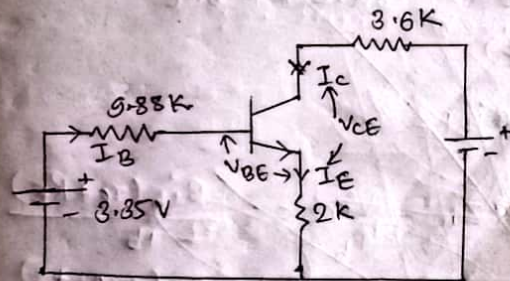



Applying KVL in input loop, we get,

$$8.35 = 9.88 I_B + V_{BE} + 2 I_E$$

$$\Rightarrow 8.35 = 9.88 I_B + 0.7 + 2 I_E$$

$$\Rightarrow 8.35 - 0.7 = \frac{9.88 I_E}{(\beta + 1)} + 2 I_E$$

$$\Rightarrow 2.65 = \frac{9.88 I_E}{2.1} + 2 I_E$$


$$\Rightarrow 2.65 = 2.1 I_E$$

$$\therefore I_E = 1.25 \text{ mA}$$

Now,

$$r_e = \frac{26 \times 10^{-3}}{1.25 \times 10^{-3}} = 20.8 \Omega = 0.02 \text{ K}\Omega$$

The re-model of given circuit is

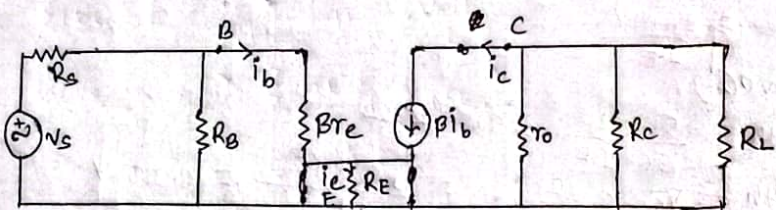

Now,

$$V_{in} = i_b R_{in} = i_b (R_B \parallel r_{in}) = i_b R_B \parallel \beta i_b (r_e + R_E)$$

$$\therefore V_{in} = \beta i_b (r_e + R_E)$$

$$V_o = i_c R_E = \beta i_b R_E$$

i) Input impedance,  $Z_{in} = \frac{V_{in}}{i_b} = \frac{\beta i_b (r_e + R_E)}{i_b}$

$$= \beta (r_e + R_E) = 90 (0.02 + 2)$$

$$\therefore Z_{in} = 181.8 \text{ K}\Omega$$

ii) Output impedance,  $Z_o = R_C \parallel R_L$

$$= \frac{R_C \times R_L}{R_C + R_L}$$

$$= \frac{3.6 \times 4}{3.6 + 4}$$

$$\therefore Z_o = 1.89 \text{ K}\Omega$$

iii) Voltage gain,  $A_v = \frac{V_o}{V_{in}} = \frac{-\beta i_b R_E}{\beta i_b (r_e + R_E)}$

$$= \frac{-R_E}{r_e + R_E}$$

$$= \frac{-2}{0.02 + 2}$$

$$\therefore A_v = 0.99 \approx 1$$

i) Input impedance,  $Z_{in} = R_B \parallel r_{in}$

we know,

$$r_{in} = \frac{\beta i_b (r_e + R_E)}{i_b} = \beta (r_e + R_E) = 90 (0.02 + 2)$$

$$= 181.8 \text{ K}\Omega$$

$$\therefore r_{in} = 181.8 \text{ K}\Omega$$

Now,

$$Z_{in} = R_B \parallel r_{in} = \frac{R_B \times r_{in}}{R_B + r_{in}}$$

$$\therefore Z_{in} = \frac{9.88 \times 181.8}{9.88 + 181.8} = 9.37 \text{ K}\Omega$$

ii) Output impedance,  $Z_o = R_C \parallel R_L$

$$= R_C \parallel R_L \quad (\because r_o = 0)$$

$$= \frac{R_C \times R_L}{R_C + R_L}$$

$$= \frac{3.6 \times 4}{3.6 + 4} = 1.89$$

$$\therefore Z_o = 1.89 \text{ K}\Omega$$



iii) Voltage gain,  $A_v = \frac{V_o}{V_{in}} = \frac{-R_E}{r_e + R_E}$

$$= \frac{-2}{0.02 + 2}$$

$\therefore A_v = -0.199$  Ans

Q. a. For the amplifier circuit given below, find


i)  $r_{in}$

ii)  $r_{out}$

iii)  $A_v$


iv)  $A_{v_s}$  (Assume  $\beta = 100$ ,  $r_e = 20 \Omega$ )

So the given amplifier circuit is:

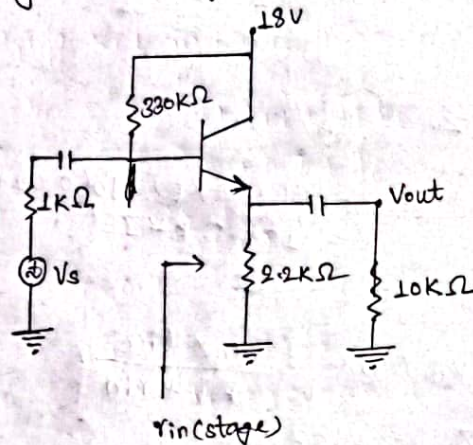


Applying KVL in

The re model of given circuit is:

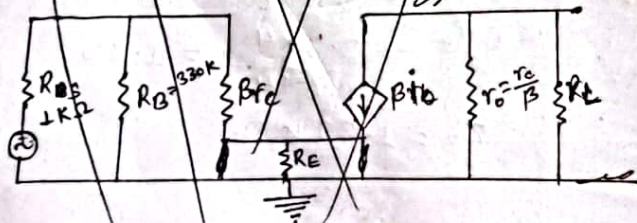

The re-model of given circuit is:

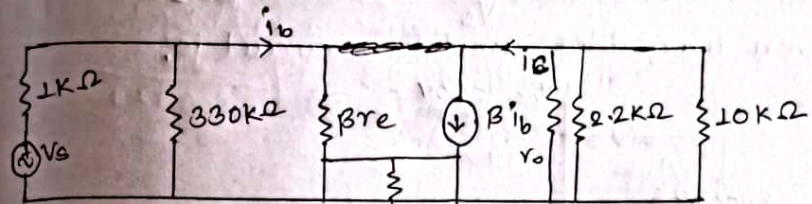

i)  $r_{in} = 1 // 330 // \beta r_e = \frac{1 \times 330}{1 + 330} // (100)(20 \times 10^{-3})$

$$= \frac{0.99 \times 20}{2.00109} = 0.621 k\Omega$$

ii)  $r_o = 2.2 // 10 = \frac{2.2 \times 10}{2.2 + 10} = 1.8 k\Omega$

iii)  $A_v = \frac{R_E}{r_e + R_E} = \frac{-2.2 \times 10^3}{20 + 2.2 \times 10^3} = 0.99 = 1$

iv)  $A_{v_s} =$

i)  $r_{in} = \beta(r_e + R_E) = 100(20 \times 10^{-3} + 2.2) = 222 k\Omega$

ii)  $r_{in(stage)} = r_{in} // R_B = \frac{222 \times 330}{222 + 330} = 132.7 k\Omega$

iii)  $r_o(stage) = r_o // R_C = R_C = 2.2 k\Omega$  ( $\because r_o \rightarrow \infty$ )

iv)  $A_v = \frac{-R_C}{r_e + R_E} = \frac{-2.2}{20 \times 10^{-3} + 2.2} = 0$


v)  $A_{v_s} = A_v \left( \frac{r_{in(stage)}}{r_s + r_{in(stage)}} \right) \cdot \left( \frac{r_o + r_{load}}{R_E} \right) \left( \frac{R_E + r_{load}}{R_{stage}} \right)$

$$= 0 \text{ Ans}$$



\* For the transistor amplifier circuit shown below, draw its re-model and find  $r_{in}$ ,  $r_{in(stage)}$ ,  $r_o(stage)$ ,  $A_v$ ,  $A_{v_s} = \frac{V_L}{V_s}$ . Assume  $\beta = 100$ .

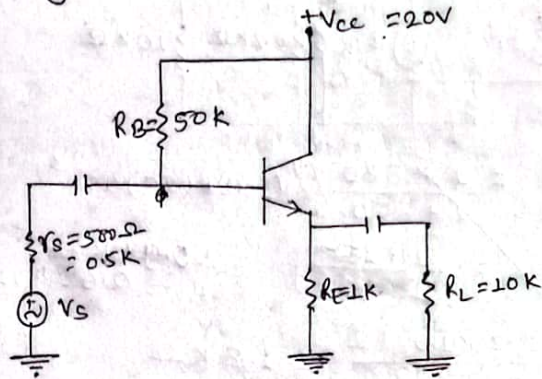Q. The given transistor amplifier circuit is:



Applying KCL in input loop, we get:

$$V_{cc} = I_B R_B + V_{BE} + I_E R_E$$

$$\Rightarrow 20 = 50 I_B + 0.7 + I_E$$

$$\Rightarrow 20 = 50 \times \frac{I_E}{(\beta+1)} + 0.7 + I_E$$

$$\Rightarrow 20 - 0.7 = \frac{50}{101} I_E + I_E$$

$$\Rightarrow 19.3 = 1.49 I_E$$


$$\therefore I_E = 12.95 \text{ mA}$$

Now,

$$r_e = \frac{26 \text{ mV}}{I_E} = \frac{26 \text{ mV}}{12.95 \text{ mA}} = 2 \Omega$$

$$\therefore r_L = R_E \parallel R_L = 1 \parallel 10 = \frac{1 \times 10}{1+10} = 0.91 \text{ k}\Omega$$

The re-model of given circuit is:-

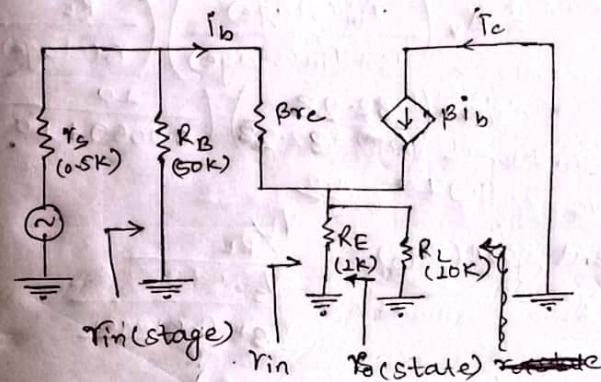

$$\text{Now, } i) r_{in} = \beta(r_e + r_L) = \beta(r_e + R_E \parallel R_L) = \beta \left( r_e + \frac{R_E \times R_L}{R_E + R_L} \right)$$

$$= 100 \left( 0.002 + \frac{1 \times 10}{1+10} \right) = 91.1 \text{ k}\Omega$$

$$ii) r_{in(stage)} = r_{in} \parallel R_B = 91.1 \parallel 50$$

$$= \frac{91.1 \times 50}{91.1 + 50} = 32.28 \text{ k}\Omega$$

$$iii) r_o(stage) = R_E \parallel \left( \frac{R_C \parallel R_B \parallel \beta r_e}{\beta} \right)$$

$$= 1 \parallel \left( \frac{0.5 \parallel 50 + 100 \times 2 \times 10^{-3}}{100} \right)$$

$$= 1 \parallel \left( \frac{\frac{0.5 \times 50}{0.5+50} + 0.2}{100} \right)$$

$$= 1 \parallel 0.00695$$

$$\therefore r_o(stage) = 0.0069 \text{ k}\Omega$$

$$iv) \text{ voltage gain, } A_v = \frac{r_L}{r_e + r_L} = \frac{0.91}{0.002 + 0.91} = 0.9978$$

Current gain:



$\Rightarrow$  Overall gain ( $A_{vs}$ ) =  $\frac{V_L}{V_s}$   
 voltage,  
 $= A_v \left( \frac{r_{in(stage)}}{r_s + r_{in(stage)}} \right) \left( \frac{R_L}{r_o(stage) + R_L} \right)$   
 $= 0.99 \left( \frac{32.28}{0.5 + 32.28} \right) \left( \frac{10}{0.0069 + 10} \right)$

$\therefore A_{vs} = 0.974$  Ans


$\Rightarrow$  Overall current gain ( $A_{is}$ ) =  $\frac{V_L / R_L}{V_s}$   
 $\frac{r_{in} + r_{in(stage)}}{R}$

$= \frac{V_L}{V_s} \times \left( \frac{r_{in} + r_{in(stage)}}{R_L} \right)$

$= 0.974 \times \left( \frac{0.5 + 32.28}{10} \right)$

$\therefore A_{is} = 3.2$  Ans

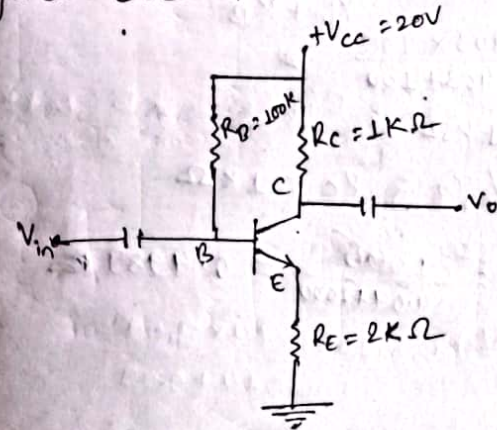2. Draw and find re model, and find  $r_{in}$ ,  $r_{in(stage)}$ ,  $r_o(stage)$ ,  $A_v$ ,  $A_{vs}$  and  $A_{is}$ . (Take  $\beta = 100$ ).  
 The given circuit is:



Applying KVL in input loop, we get:-

$V_{CC} = 100 I_B + V_{BE} + I_E R_E$

$\Rightarrow 20 = 100 \frac{I_E}{101} + 0.7 + 2 I_E$

$\Rightarrow 20 - 0.7 = 2.99$


$\therefore \frac{19.3}{2.99} = I_E$

$\therefore I_E = 6.45 \text{ mA}$

Now,

$r_e = \frac{26 \text{ mV}}{6.45 \text{ mA}} = 4.03 \Omega = 0.00403 \text{ k}\Omega$

The re-model of given circuit is:

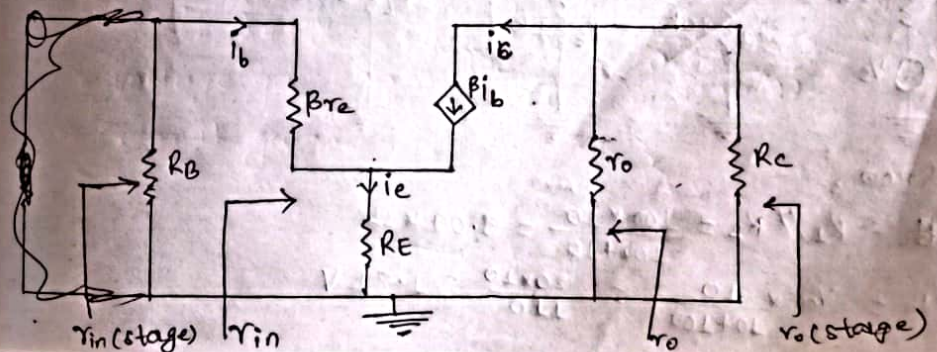



$$i) r_{in} = \beta(r_e + R_E) = 100(0.00403 + 2) = 200.403 \text{ K}\Omega$$

$$ii) r_{in(stage)} = r_{in} // R_B = \frac{r_{in} \times R_B}{r_{in} + R_B}$$

$$= \frac{200.403 \times 100}{200.403 + 100}$$

$$= 66.71 \text{ K}\Omega$$

$$iii) r_o(stage) = R_c // r_o = R_c = 1 \text{ K}\Omega$$


$$iv) A_v = -\frac{R_c}{r_e + R_E} = \frac{-1000}{0.00403 + 2000} = 0.4989$$

$$iv) A_{v_s} = \frac{V_L}{V_s}$$

$$= A_v \left( \frac{r_{in(stage)}}{r_{in(stage)} + r_s} \right)$$

Q.8. Draw re-model and find  $r_{in}$ ,  $r_{in(stage)}$ ,  $r_o(stage)$ ,  $A_v$ ,  $\frac{V_L}{V_s}$  and  $\frac{i_L}{i_s}$ . Take  $\beta = 100$

sg The given circuit is:

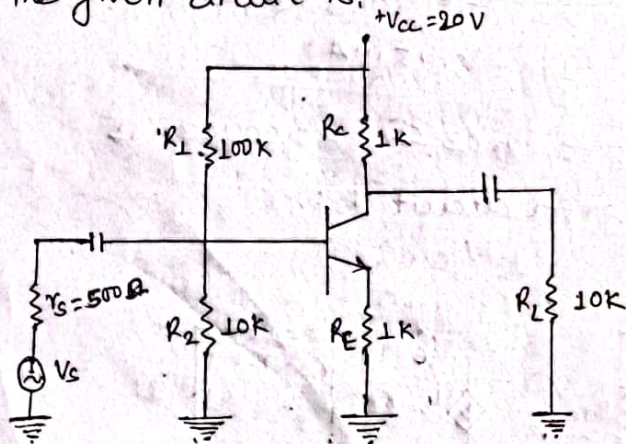


we know,

$$R_B = R_{Th} = R_1 // R_2 = \frac{100 \times 10}{100 + 10} = 9.09 \text{ K}\Omega$$

$$V_{Th} = V_{cc} \times \frac{10}{10 + 100} = \frac{20 \times 10}{110} = 1.81 \text{ V}$$

The Thevenin's equivalent circuit is:

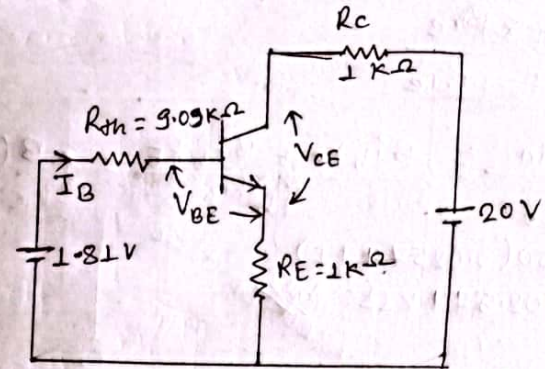

Applying KVL in input loop, we get:

$$1.81 = 9.09 I_B + 0.7 + I_E$$

$$\Rightarrow 1.81 - 0.7 = 9.09 \times \frac{I_E}{100} + I_E$$


$$\Rightarrow \frac{1.11}{1.0909} = I_E$$

$$\therefore I_E = 1.01 \text{ mA}$$

Now,

$$\therefore r_e = \frac{26 \text{ mV}}{1.01 \text{ mA}} = 25.74 \Omega = 0.02574 \text{ K}\Omega$$

The re-model of given circuit is:

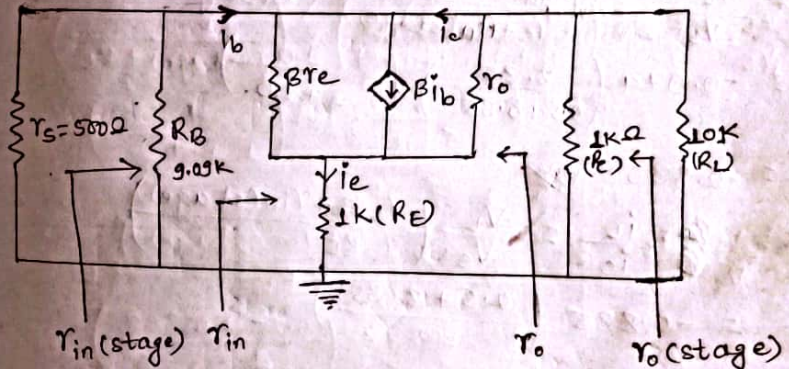

$$\therefore \beta r_e =$$



$$i) r_{in} = R_B \parallel R_E$$

$$i) r_{in} = \frac{v_{in}}{i_b} = \frac{\beta i_b r_e + \beta i_b R_E}{i_b} = \beta (r_e + R_E)$$

$$= 100(0.02574 + 1)$$

$$\therefore r_{in} = 102.574 \text{ k}\Omega$$

$$ii) r_{in(stage)} = r_{in} \parallel R_B = \frac{102.574 \times 9.09}{102.574 + 9.09}$$

$$= 8.35 \text{ k}\Omega$$

$$iii) r_o(stage) = R_C \parallel r_o = R_C \quad (\because R_C \parallel r_o = R_C)$$

$$= 1 \text{ k}\Omega$$

$$iv) A_v = \frac{v_o}{v_i} = \frac{-R_C}{r_e + R_E} = \frac{-1}{0.02574 + 1}$$

$$= -0.974$$

$$v) A_{v_s} = \frac{V_L}{V_s} = A_v \left( \frac{r_{in(stage)}}{r_s + r_{in(stage)}} \right) \left( \frac{R_L}{r_o(stage) + R_L} \right)$$

$$= -0.974 \left( \frac{8.35}{0.5 + 8.35} \right) \left( \frac{10}{1 + 10} \right)$$

$$= -0.835$$

$$vi) A_{i_s} = \frac{i_L}{i_s} = \frac{V_L}{V_s} \left( \frac{r_s + r_{in(stage)}}{R_L} \right)$$


$$= -0.835 \left( \frac{0.5 + 8.35}{10} \right)$$

$$= -0.73$$

## Emitter bypassed

Q. For the transistor amplifier circuit shown below, find its  $r_e$ -model and  $r_{in}$ ,  $r_{in(stage)}$ ,  $A_v$  (stage),  $A_{v_s}$ ,  $\frac{V_L}{V_s}$  and also find the value of  $V_L$  if  $V_s = 100$ . Assume  $\beta = 100$ .

The given amplifier circuit is:

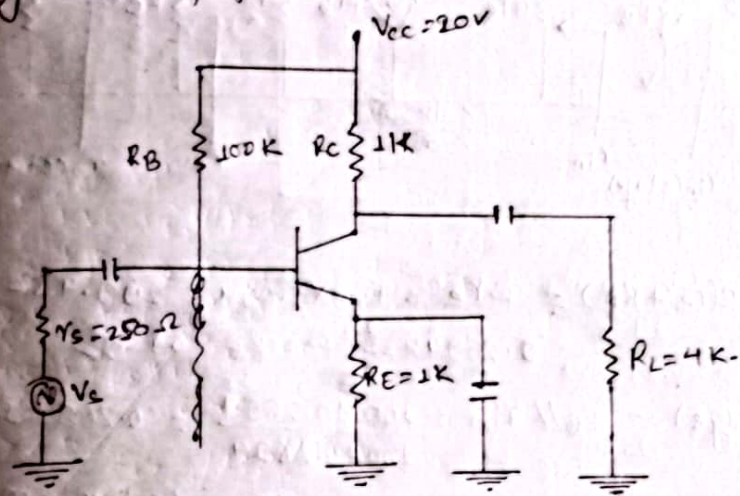

Applying KVL in input loop, we get:

$$V_{cc} = I_B R_B + V_{BE} + I_E R_E$$

$$\Rightarrow 20 = 100 I_B + 0.7 + I_E$$

$$\Rightarrow 20 - 0.7 = 100 \frac{I_E}{100} + I_E$$

$$\Rightarrow 19.3 = 2 I_E$$

$$\therefore I_E = 9.65 \text{ mA}$$


Now,

$$r_e = \frac{26 \text{ mV}}{9.65 \text{ mA}} = 2.694 \Omega$$

$$\therefore \beta r_e = 100 \times 2.694 = 0.2694 \text{ k}\Omega$$



The re-model of given circuit is:-

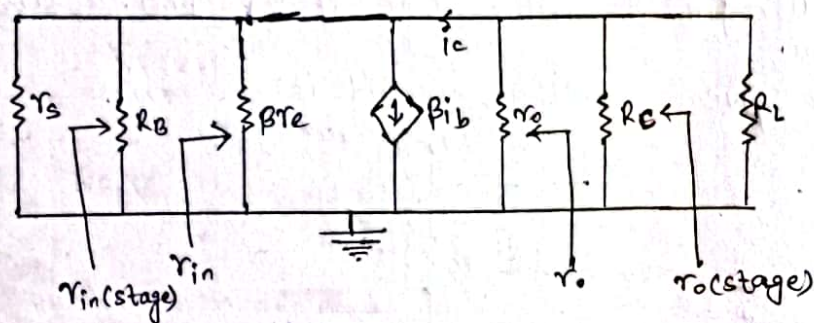

$$i) r_{in} = \beta(r_e + R_E) = \beta r_e = 100 \times 2.694 = 269.4 \Omega$$

$$= 0.2694 \text{ k}\Omega \quad (\because R_E = 0) \text{ Ans}$$

$$ii) r_{in(stage)} = R_B // r_{in} = \frac{100 \times 0.2694}{100 + 0.2694} = 0.268 \text{ k}\Omega \text{ Ans}$$

$$iii) r_{o(stage)} = R_C // r_o = R_C = 1 \text{ k}\Omega \quad (\because r_o = \infty)$$

$$iv) A_v = \frac{-R_C}{r_e + R_E} = \frac{-R_C}{r_e} = \frac{-1 \times 10^3}{2.694} = -371.2 \text{ Ans}$$

$$v) A_{vs} = \frac{V_L}{V_s} = A_v \left( \frac{r_{in(stage)}}{r_s + r_{in(stage)}} \right) \times \left( \frac{R_L}{r_{o(stage)} + R_L} \right)$$

$$= -371.2 \left( \frac{0.268}{0.25 + 0.268} \right) \times \left( \frac{4}{1 + 4} \right)$$

$$= -153.639 \text{ Ans}$$

$$vi) A_{ic} = \frac{i_L}{i_c} = \frac{V_L}{V_c} \times \left( \frac{r_s + r_{in(stage)}}{R_L} \right)$$

$$= -153.639 \times \left( \frac{0.25 + 0.268}{4} \right)$$

$$= -10.896 \text{ Ans}$$

we know,

$$V_s = 100,$$

now,

$$\frac{V_L}{V_s} = -153.639$$


$$\therefore V_L = -153.639 \times 100 \text{ (V)}$$

$$\therefore V_L = -15363.9 \text{ V}$$

Pre-Board - 2079

4.a. For the given common emitter amplifier, find the following using re model. Input impedance, output impedance, voltage gain,  $\beta = 100$ ,  $V_{CC} = +12 \text{ V}$ .

The given CE amplifier circuit is:-

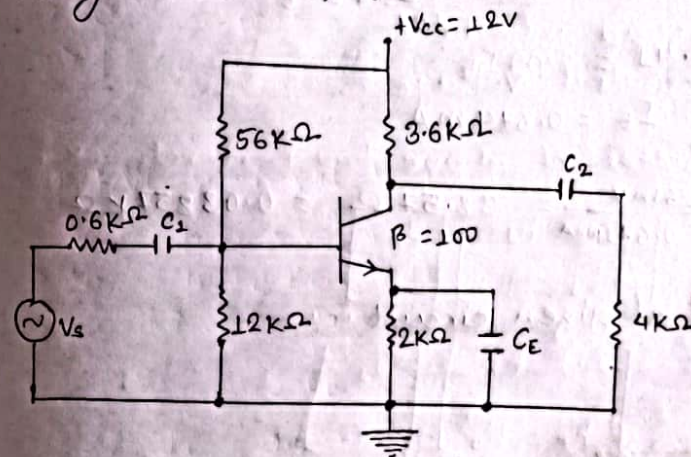


Here,

$$R_B = R_{th} = R_1 // R_2 = \frac{56 \times 12}{56 + 12} = 9.88 \text{ k}\Omega$$

$$V_{th} = V_{CC} \times \frac{R_2}{R_1 + R_2} = 12 \times \frac{12}{12 + 56} = 2.11 \text{ V}$$



The thevenin's equivalent circuit is:

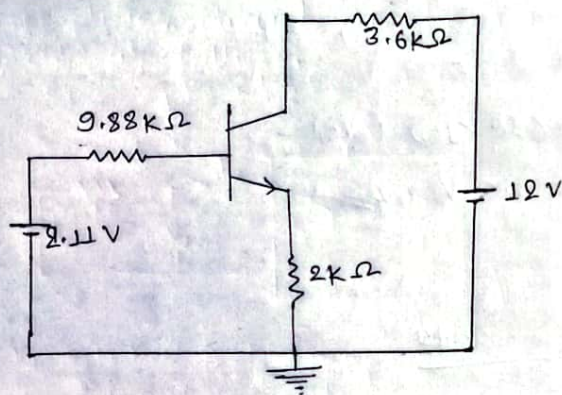

Applying KVL in input loop, we get:

$$2.11 = 9.88 I_B + 0.7 + 2 I_E$$


$$\Rightarrow 2.11 - 0.7 = 9.88 \times \frac{I_E}{101} + 2 I_E$$

$$\Rightarrow 1.41 = 2.09 I_E$$

$$\therefore I_E = 0.674 \text{ mA}$$

$$\text{Now, } r_e = \frac{26 \text{ mV}}{0.674 \text{ mA}} = 38.57 \Omega = 0.03857 \text{ k}\Omega$$

The  $r_e$  model of given circuit is:

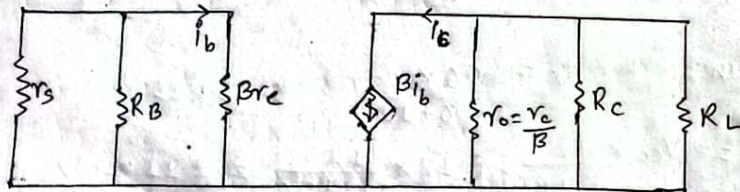

$$r_{in} = \beta r_e = 100 \times 0.03857 = 3.857 \text{ k}\Omega$$

$$\begin{aligned} \text{i) Input impedance, } Z_{in} &= r_{in} \parallel R_B = \frac{r_{in} \times R_B}{r_{in} + R_B} \\ &= \frac{3.857 \times 9.88}{3.857 + 9.88} \\ &= 2.774 \text{ k}\Omega \end{aligned}$$


$$\begin{aligned} \text{ii) Output Impedance, } Z_o &= r_o \parallel R_c = R_c \quad (\because r_o = \infty) \\ &= 3.6 \text{ k}\Omega \end{aligned}$$

$$\text{iii) } A_v = -\frac{R_c}{r_e} = -\frac{3.6}{0.03857} = -93.33$$


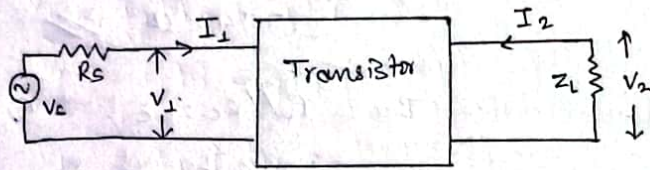
## Hybrid Parameters

A BJT amplifier circuit can be represented by two port network are as follows:



Here,  $V_1$  = input voltage  
 $I_1$  = input current  
 $R_s$  = source resistance  
 $V_s$  = source voltage  
 $I_2$  = output current  
 $Z_L$  = load impedance  
 $V_2$  = output voltage

The h-parameters of above two port network is:

$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

$$\Rightarrow \begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_i & h_r \\ h_f & h_o \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

where,  
 $h_{11} = h_i$  = input impedance (resistance)  
 $h_{12} = h_r$  = reverse voltage gain  
 $h_{21} = h_f$  = forward voltage gain  
 $h_{22} = h_o$  = output admittance

$$\Rightarrow V_1 = h_i I_1 + h_r V_2 \quad \text{--- (1)}$$

$$I_2 = h_f I_1 + h_o V_2 \quad \text{--- (2)}$$

from above two port network,

$$V_2 = -I_2 Z_L \quad \text{--- (3)}$$

The h-model of above two port network is:

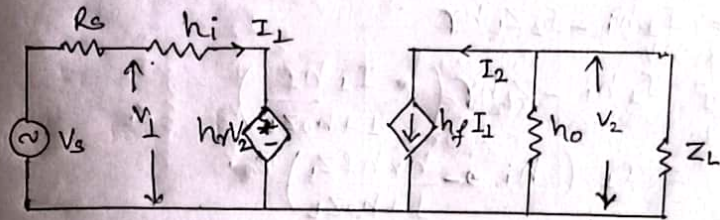


fig. h-model of two port network

i) Current gain,  $A_i = -\frac{I_2}{I_1}$

from (2),

$$I_2 = h_f I_1 + h_o V_2$$

$$\Rightarrow I_2 = h_f I_1 + h_o (-I_2 Z_L) \quad (\because \text{from (3)})$$

$$\Rightarrow I_2 + I_2 h_o Z_L = h_f I_1$$

$$\Rightarrow \frac{I_2}{I_1} = \frac{h_f}{1 + h_o Z_L}$$

$$\therefore A_i = -\frac{I_2}{I_1} = -\frac{h_f}{1 + h_o Z_L}$$

ii) voltage gain,  $A_v = \frac{V_2}{V_1} = -\frac{I_2 Z_L}{V_1}$

$$= \frac{-A_i I_1 Z_L}{V_1}$$

$$= \frac{-A_i Z_L}{V_1 / I_1} = \frac{-A_i Z_L}{Z_i}$$

$$\therefore A_v = \frac{-A_i Z_L}{Z_i}$$



iii) Input impedance,  $Z_i = \frac{V_1}{I_1}$

from (1),

$$V_1 = I_1 h_i + h_r V_2 = I_1 h_i + h_r (-I_2 Z_L)$$

$$\Rightarrow V_1 = I_1 h_i - I_2 Z_L h_r$$

$$\Rightarrow V_1 = I_1 h_i - Z_L h_r \left( \frac{I_1 h_f}{1 + h_o Z_L} \right)$$

$$\Rightarrow V_1 = I_1 \left( h_i - \frac{h_r h_f Z_L}{1 + h_o Z_L} \right)$$

$$\Rightarrow \frac{V_1}{I_1} = h_i - \frac{h_r h_f}{\frac{1}{Z_L} + h_o}$$

$$\therefore \frac{V_1}{I_1} = h_i - \frac{h_r h_f}{Y_L + h_o}$$

iv) Output admittance,  $Y_o = \frac{I_2}{V_2}$

From (2),

$$I_2 = h_f I_1 + h_o V_2$$

$$\Rightarrow I_2 = \frac{h_f I_1}{1 + h_o Z_L} + h_o V_2$$

$$\Rightarrow I_2 = I_2 (1 + h_o Z_L) + h_o V_2$$

$$\Rightarrow (1 - 1 - h_o Z_L) I_2 = h_o V_2$$

$$\Rightarrow \frac{I_2}{V_2} = \frac{h_o}{-h_o Z_L} = -\frac{1}{Z_L}$$

$$\therefore Y_o = -\frac{1}{Z_L}$$

Again,

from (2),  $I_2 = h_f I_1 + h_o V_2$

$$\Rightarrow \frac{I_2}{V_2} = \frac{h_f I_1}{V_2} + h_o$$

$$\Rightarrow Y_o = h_o + h_f \frac{I_1}{V_2} \quad \text{--- (a)}$$

from (2) & (3), we get;

$$\frac{-V_2}{Z_L} = h_f I_1 + h_o V_2$$

$\Rightarrow$

Applying KVL in input loop, we get:

$$V_s = I_1 R_s + h_i I_1 + h_r V_2$$

$$\Rightarrow 0 = I_1 (h_i + R_s) + h_r V_2$$

$$\Rightarrow -h_r V_2 = I_1 (h_i + R_s)$$

$$\therefore \frac{I_1}{V_2} = -\frac{h_r}{h_i + R_s}$$

From (a),


$$Y_o = h_o - \frac{h_r h_f}{h_i + R_s}$$

$$\therefore Z_o = \frac{1}{Y_o}$$


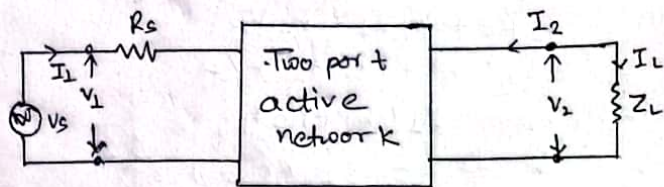
## h-parameters or h-model parameters

A BJT amplifier circuit can be represented by two port network as follows:



Here,  
 $I_1$  = input current  
 $V_1$  = input voltage  
 $R_s$  = source resistance  
 $V_s$  = voltage source voltage  
 $I_2$  = output current  
 $V_2$  = output voltage  
 $I_L$  = load current  
 $Z_L$  = Load impedance

The h-parameters of above two port network is:-

$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

$$\Rightarrow \begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_i & h_r \\ h_f & h_o \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

where,  
 $h_{11} = h_i$  = input impedance (resistance)  
 $h_{12} = h_r$  = reverse voltage gain  
 $h_{21} = h_f$  = forward voltage gain  
 $h_{22} = h_o$  = output admittance

$$\Rightarrow V_1 = h_i I_1 + h_r V_2 \quad \text{--- (1)}$$

$$I_2 = h_f I_1 + h_o V_2 \quad \text{--- (2)}$$

From output loop of two port network,

$$V_2 = -I_2 Z_L \quad \text{--- (3)}$$

From input loop of two port network,

The h-model of two port network is:-

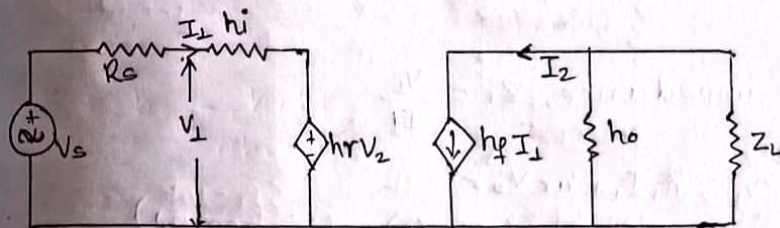


fig. h-model of two port network

i) Input impedance,  $Z_i = \frac{V_1}{I_1}$

ii) Current gain,  $A_i = -\frac{I_2}{I_1}$

From (2),

$$\begin{aligned} V_1 &= h_i I_1 + h_r V_2 \\ \Rightarrow V_1 &= h_i I_1 - I_2 Z_L h_o \quad \text{--- (3)} \\ \Rightarrow I_2 &= h_f I_1 + h_o V_2 \\ \Rightarrow I_2 &= h_f I_1 - I_2 Z_L h_o \\ \Rightarrow I_2 + I_2 Z_L h_o &= h_f I_1 \\ \Rightarrow I_2 (1 + Z_L h_o) &= h_f I_1 \\ \Rightarrow \frac{I_2}{I_1} &= \frac{h_f}{1 + Z_L h_o} \end{aligned}$$

$$\therefore A_i = -\frac{I_2}{I_1} = -\frac{h_f}{1 + Z_L h_o}$$



ii) voltage gain,  $A_v = \frac{V_2}{V_1} = \frac{-I_2 Z_L}{V_1}$  ( $\because$  from (3))

$$= \frac{-I_2 Z_L}{V_1} = \frac{-Z_L \times I_1 A_i}{V_1}$$

$$\cancel{A_v} = \frac{-A_i Z_L}{V_1 / I_1}$$

$$\therefore A_v = -\frac{A_i Z_L}{Z_i}$$

iii) Input impedance,  $Z_i = \frac{V_1}{I_1}$

From (1),

$$V_1 = h_i I_1 + h_r V_2$$

$$\Rightarrow V_1 = h_i I_1 + h_r (-I_2 Z_L) \quad (\because \text{from (3)})$$

$$\Rightarrow V_1 = h_i I_1 - h_r Z_L I_2$$

$$\Rightarrow V_1 = h_i I_1 - h_r Z_L \left( \frac{h_f}{1 + Z_L h_o} \right)$$

$$\Rightarrow V_1 = I_1 \left( h_i - \frac{h_r h_f}{\frac{1}{Z_L} + h_o} \right)$$

$$\therefore \frac{V_1}{I_1} = h_i - \frac{h_r h_f}{h_o + Y_L}$$

$$\therefore Z_i = h_i - \frac{h_r h_f}{h_o + Y_L}$$

iv) Output admittance ( $Y_o$ ) and Input-output impedance  $Z_o$ :

$$Z_o = \frac{V_2}{I_2}$$

From (2),

$$I_2 = h_f I_1 + h_o V_2$$

$$\Rightarrow \frac{I_2}{V_2} = h_f \frac{I_1}{V_2} + h_o$$

$$\therefore Z_o = h_o + h_f \frac{I_1}{V_2} \quad \text{--- (a)}$$

Applying KVL in input loop of h-model, we get:

$$V_s = I_1 R_s + I_1 h_i + V_2 h_r$$

$$\Rightarrow 0 = I_1 (R_s + h_i) + V_2 h_r$$

$$\Rightarrow -V_2 h_r = I_1 (R_s + h_i)$$

$$\therefore \frac{I_1}{V_2} = -\frac{h_r h_f}{R_s + h_i}$$

from (a),


$$Y_o = h_o - \frac{h_r h_f}{R_s + h_i}$$

$$\therefore Z_o = \frac{1}{Y_o}$$



## Numericals:

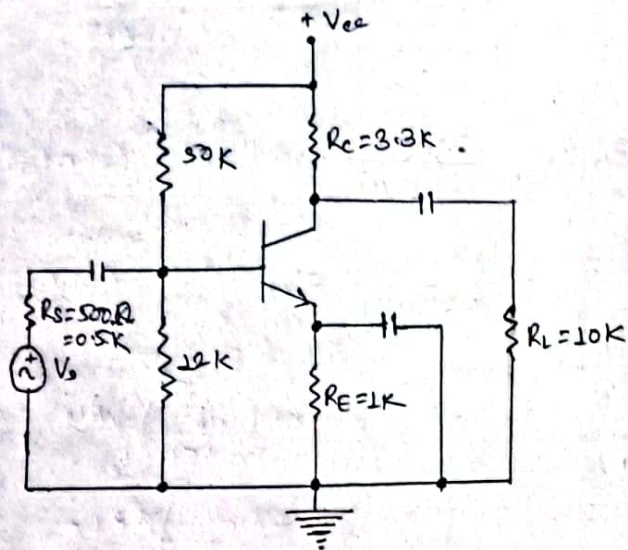1. For the given transistor amplifier circuit the h-parameters are  $h_{ie} = 1600 \Omega$ ,  $h_{fe} = 80$ ,  $h_{re} = 20 \times 10^{-4}$ , and  $h_{oe} = 20 \times 10^{-6}$ . Find  $Z_i$ ,  $Z_{i(\text{stage})}$ ,  $Z_o$ ,  $Z_{o(\text{stage})}$ ,  $A_i$ ,  $A_v$ ,  $A_{v_s}$ .
- The given amplifier circuit is:



Given:


$$h_{ie} = 1600 \Omega = 1.6 \text{ k}\Omega$$

$$h_{fe} = 80$$

$$h_{re} = 20 \times 10^{-4}$$

$$h_{oe} = 20 \times 10^{-6} \text{ S}$$

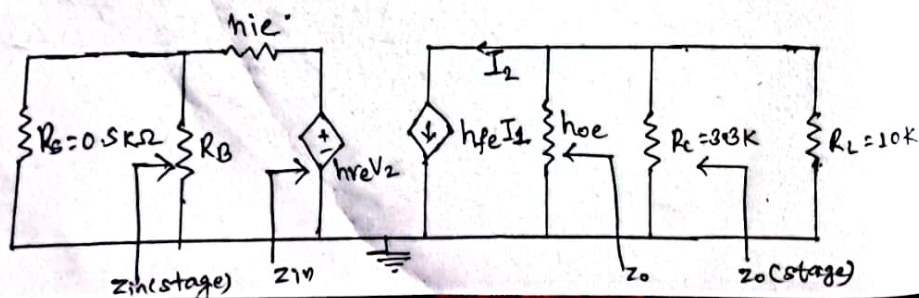The h-model of given two port network is:



$$V_1 = h_{ie} I_1 + h_{re} V_2$$

$$I_2 = h_{fe} I_1 + h_{oe} V_2$$

we know,

$$Z_L = R_C / R_L = \frac{R_C \times R_L}{R_C + R_L} = \frac{3.3 \times 10}{3.3 + 10} = 2.48 \text{ k}\Omega$$

$$R_B = R_1 / R_2 = \frac{50 \times 12}{50 + 12} = 9.67 \text{ k}\Omega$$

i) Input impedance,  $Z_{in} = h_{ie} - \frac{h_{fe} \cdot h_{re}}{h_{oe} + \frac{1}{Y_o}}$

$$= 1.6 \text{ k}\Omega - \frac{80 \times 20 \times 10^{-4}}{20 \times 10^{-6} + \frac{1}{2.48}}$$

$$\therefore Z_{in} = 1.2 \text{ k}\Omega$$

ii) Output impedance,  $Z_o = \frac{1}{Y_o}$

we know,

$$Y_o = h_{oe} - \frac{h_{fe} \cdot h_{re}}{h_{ie} + (R_s / R_B)}$$

$$\Rightarrow Y_o = 20 \times 10^{-6} - \frac{80 \times 20 \times 10^{-4}}{(1.6 + \frac{0.5 \times 9.67}{0.5 + 9.67}) \times 10^{-3}}$$

$$\Rightarrow Y_o = 20 \times 10^{-6} - 0.77 \times 10^{-6}$$

$$\Rightarrow Y_o = -5.7 \times 10^{-5}$$

$$\therefore Y_o = 5.7 \times 10^{-5} \quad (\text{neglecting negative sign})$$

Now,

$$Z_o = \frac{1}{5.7 \times 10^{-5}} = 17.543 \text{ k}\Omega$$



$$\text{iii)} A_{oi} = \frac{-h_{fe}}{1+h_{oe}Z_L} = \frac{-80}{1+20 \times 10^{-6} \times 24.8 \times 10^3}$$

$$= -76.22 \quad \text{Ans}$$

$$\text{iv)} A_v = \frac{-A_i Z_L}{Z_{in}} = \frac{-76.22 \times 2.48}{1.2} = -157.52 \quad \text{Ans}$$

$$\text{v)} Z_{in}(\text{stage}) = Z_{in} \parallel R_B = \frac{1.2 \times 9.67}{1.2 + 9.67} = 1.067 \text{ K}\Omega \quad \text{Ans}$$

$$\text{vi)} Z_o(\text{stage}) = Z_o \parallel R_c = \frac{17.543 \times 3.3}{17.543 + 3.3}$$

$$= 2.77 \text{ K}\Omega \quad \text{Ans}$$

$$\text{vii)} A_{vs} = A_v \left( \frac{Z_{in}(\text{stage})}{R_s + Z_{in}(\text{stage})} \right) \times \left( \frac{R_L}{R_L + Z_o(\text{stage})} \right)$$

$$= -157.52 \left( \frac{1.067}{0.5 + 1.067} \right) \times \left( \frac{10}{10 + 2.77} \right)$$

$$\therefore A_{vs} = -83.99 \quad \text{Ans}$$

$$\text{viii)} A_{is} = A_{vs} \left( \frac{R_s + Z_{in}(\text{stage})}{R_L} \right)$$

$$= -83.99 \left( \frac{0.5 + 1.067}{10} \right)$$

$$\therefore A_{is} = 13.16 \quad \text{Ans}$$

1. The transistor shown in figure below has following h-parameters are  $h_{ie} = 1 \text{ K}\Omega$ ,  $h_{re} = 2.5 \times 10^{-4}$ ,  $h_{fe} = 50$ ,  $h_{oe} = 25 \mu\text{S}$ . Find

i) input impedance,  $Z_{in}$


ii) output impedance,  $Z_{out}$

iii) voltage gain,  $A_v$

iv) Current gain,  $A_i$

2013-Fall

Sol The given transistor is:

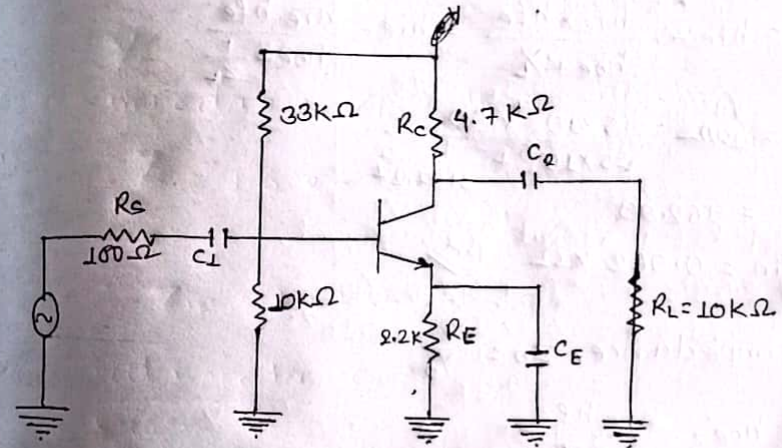

Given:-


$$h_{ie} = 1 \text{ K}\Omega$$

$$h_{re} = 2.5 \times 10^{-4}$$

$$h_{fe} = 50$$

$$h_{oe} = 25 \mu\text{S} = 25 \times 10^{-6} \text{ S}$$

The h-model of given transistor is:

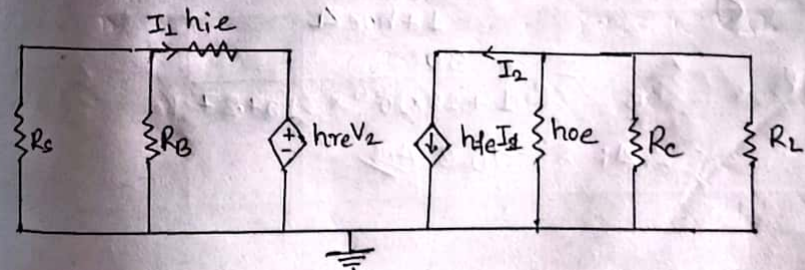



Now,  $R_B = R_1 / R_2 = \frac{10 \times 33}{10 + 33} = 7.674 \text{ K}\Omega = 7674.4 \Omega$

$Z_L = R_C / R_L = \frac{4.7 \times 10}{4.7 + 10} = 3.197 \text{ K}\Omega = 3197.27 \Omega$

$Z_B = R_S // R_B = \frac{100 \times 7674.4}{100 + 7674.4} = 98.71 \Omega$

i) Input impedance,  $Z_{in}$ :

$$Z_{in} = h_{ie} - \frac{h_{re} \times h_{fe}}{h_{oe} + \frac{1}{Z_L}} = h_{ie} - \frac{h_{re} h_{fe}}{h_{oe} + \frac{1}{Z_L}}$$

$$= 1000 - \frac{2.5 \times 10^{-4} \times 50}{25 \times 10^{-6} + \frac{1}{3197.27}}$$

$$= 962.99$$

$\therefore Z_{in} = 0.962 \text{ K}\Omega$

ii) Output impedance,  $Z_o = \frac{1}{Y_o}$

Now,  $Y_o = h_{oe} - \frac{h_{re} h_{fe}}{h_{ie} + Z_B}$

$$= 25 \times 10^{-6} - \frac{2.5 \times 10^{-4} \times 50}{1000 + 98.71}$$

$$\therefore Y_o = 1.36 \times 10^{-5}$$

$\therefore Z_o = \frac{1}{Y_o} = \frac{1}{1.36 \times 10^{-5}} = 7.33 \times 10^4 = 73.33 \text{ K}\Omega$

iii) Voltage gain,

iv) Current gain,  $A_i = - \frac{h_{fe}}{1 + h_{oe} Z_L}$

$$= - \frac{50}{1 + 25 \times 10^{-6} \times 3197.27}$$

$$\therefore A_i = -46.3$$

iii) Voltage gain,  $A_v = \frac{A_i Z_L}{Z_{in}}$

$$= \frac{-46.3 \times 3197.27}{962.99}$$

$$\therefore A_v = -153.72$$

v) Voltage gain with  $R_S$ ;  $A_{vs}$ :

$$A_{vs} = A_i \times \frac{Z_{in}}{Z_{in} + Z_S}$$

$$= -153.72 \times \frac{962.99}{962.99 + 98.71}$$

$$\therefore A_{vs} = -139.42$$

2014-Pall

2. For the CE amplifier, find the following using re-model


i) input impedance,  $Z_{in}$

ii) Output impedance,  $Z_o$

iii) Current gain,  $A_i$

iv) Voltage gain,  $A_v$  (Assume  $\beta = 100$ ,  $V_{CC} = +20V$ )

The given CE amplifier circuit is:

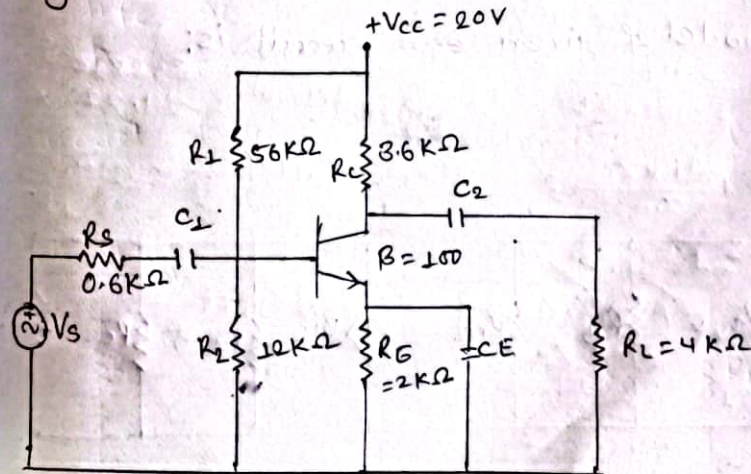




~~Given~~

$$R_B = R_{Th} = R_1 \times R_2 / (R_1 + R_2) = \frac{12 \times 56}{12 + 56} = 9.88 \text{ K}\Omega$$

$$V_{Th} = V_{CC} \times \frac{12}{12 + 56} = 20 \times \frac{12}{12 + 56} = 3.59 \text{ V}$$

The Thevenin's equivalent circuit is:

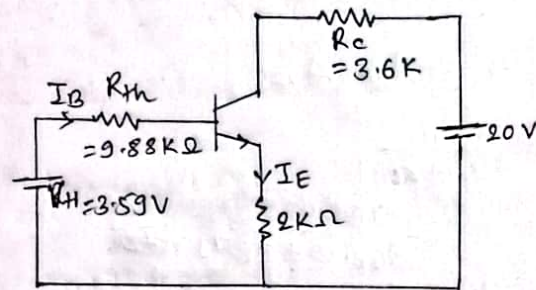


Applying KVL in input loop, we get;

$$\begin{aligned} 3.59 &= 9.88 I_B + 0.7 + 2 I_E \\ \Rightarrow 3.59 - 0.7 &= 9.88 \frac{I_E}{100} + 2 I_E \\ \Rightarrow 2.89 &= 2.09 I_E \\ \therefore I_E &= 1.38 \text{ mA} \end{aligned}$$

Now,

$$r_e = \frac{26 \text{ mV}}{1.38 \text{ mA}} = 18.84 \Omega = 0.01884 \text{ K}\Omega$$

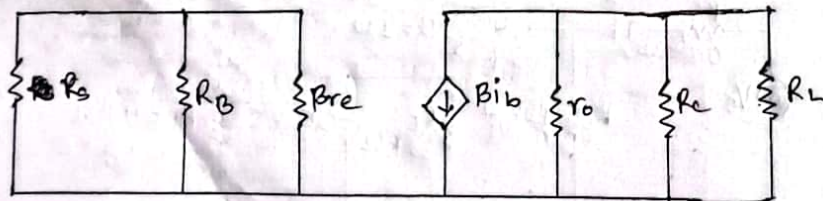The re model of given ~~circuit~~ circuit is:



$$\begin{aligned} \text{i) Input impedance, } Z_{in} &= R_B \parallel \beta r_e = \frac{100 \times 0.01884 \times 9.88}{100 \times 0.01884 + 9.88} \\ \therefore Z_{in} &= \frac{1.884}{1.01884} \text{ K}\Omega \end{aligned}$$

$$\begin{aligned} \text{ii) Output impedance, } Z_o &= r_o \parallel R_C \parallel R_L = R_C \parallel R_L \\ &= 3.6 \parallel 4 \\ &= \frac{3.6 \times 4}{3.6 + 4} \\ \therefore Z_o &= 1.894 \text{ K}\Omega \end{aligned}$$

$$\text{iii) Voltage gain, } A_v = -\frac{R_C}{r_e} = -\frac{3.6}{0.01884} = -191.08 \text{ Ans}$$


$$\text{iv) Current gain, } \beta A_1 = \beta = -100 \text{ Ans}$$

20.5 - Fall

Q Find  $A_{vs}$ ,  $A_v$ ,  $Z_o$ ,  $Z_{in}$  of the following circuit. Diagram using h-parameters


$$h_{fe} = 100, h_{ie} = 1.175 \text{ K}\Omega, h_{oe} = 20 \mu\text{A/V}$$

Q The given circuit diagram is:

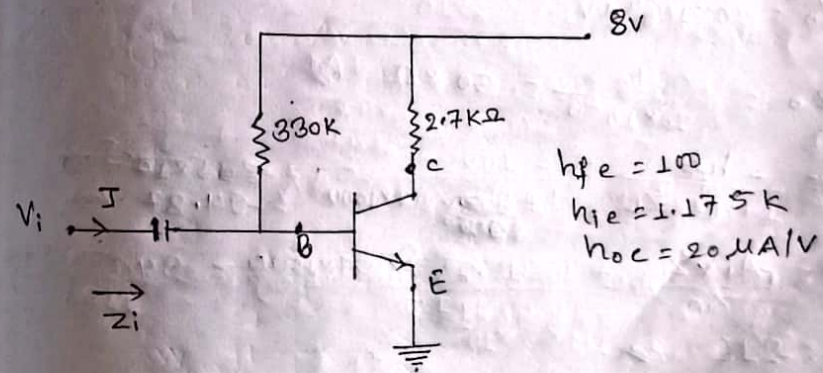



The h-model of given circuit is,

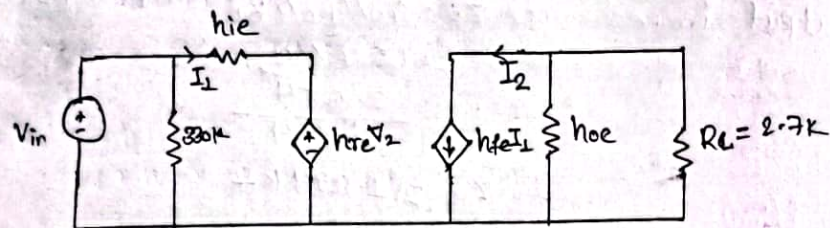

$$i) Z_{in} = h_{ie} - \frac{h_{fe} h_{re}}{h_{oe} + \frac{1}{Y_L}} = h_{ie} - \frac{h_{fe} h_{re}}{h_{oe} + \frac{1}{Y_L}}$$

$$= 1.175 \times 1000 - \frac{0}{20 \times 10^{-6} + \frac{1}{R_L}}$$

$$\therefore Z_{in} = 1.175 k\Omega$$

$$ii) Z_o = \frac{1}{Y_o}$$

$$\text{Now, } Y_o = h_{oe} - \frac{h_{re} h_{fe}}{Z_{in} + h_{ie}} = 20 \times 10^{-6} A/V - 0$$

$$\therefore Y_o = 20 \times 10^{-6} A/V$$

$$\therefore Z_o = \frac{1}{20 \times 10^{-6}} = 50 k\Omega$$

$$iii) A_v = \frac{-h_{fe}}{1 + h_{oe} Z_L} = \frac{-100}{1 + \frac{20 \times 10^{-6} \times 2.7 \times 1000}{20 \times 10^{-6}}} = -94.87$$

$$iv) A_v = \frac{-A_i \times Z_L}{Z_{in}} = \frac{-94.87 \times 2.7 \times 1000}{1175} = -218$$

$$v) A_{vs} = A_v \times \left( \frac{Z_{in}}{Z_{in} + Z_s} \right) = -218 \times \frac{1175}{1175 + 0} = -218$$

2021-Spring

4.b. For the network given, determine the following parameters using the complete hybrid equivalent model.


i)  $Z_{in}$  and  $Z_{out}$

ii)  $A_v$

iii)  $A_i = I_o / I_i$

iv)  $Z_o$  &  $Z_i$

The given network is:

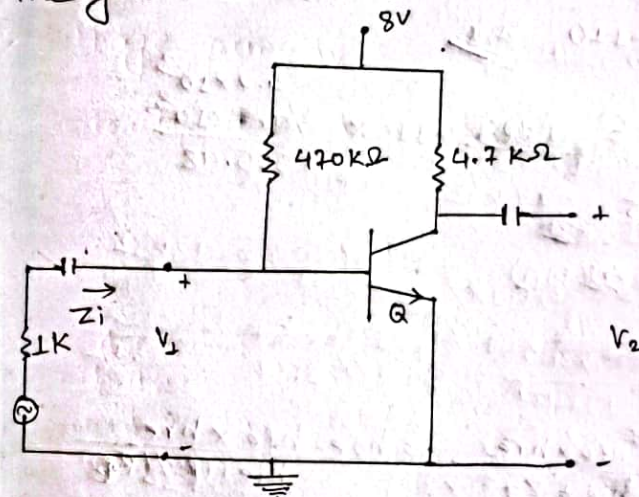


$$h_{fe} = 100$$

$$h_{ie} = 1.6 k\Omega = 1600 \Omega$$

$$h_{re} = 2 \times 10^{-4}$$

$$h_{oe} = 20 \mu A/V^{-1} = 20 \times 10^{-6} A/V^{-1}$$

The hybrid model of given network is:

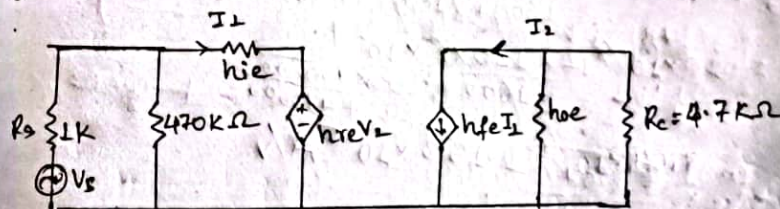

$$i) \text{ Input impedance, } Z_{in} = h_{ie} - \frac{h_{fe} h_{re}}{h_{oe} + \frac{1}{Y_L}} = h_{ie} - \frac{h_{fe} h_{re}}{h_{oe} + \frac{1}{Y_L}}$$

$$= 1600 - \frac{100 \times 2 \times 10^{-4}}{20 \times 10^{-6} + \frac{1}{4.7 \times 10^3}}$$

$$\therefore Z_{in} = 1505.48 \Omega$$



$$Z_{in} = R_{ss} || Z_{in}$$

$$= \frac{1000 \times 1505.48}{1000 + 1505.48}$$

$$\therefore Z_{in} = 600.874 \Omega \text{ Any}$$

$$ii) A_i = -\frac{h_{fe}}{1 + h_{oe} \times Z_L} = \frac{-110}{1 + 20 \times 10^{-6} \times \frac{1}{4.7 \times 10^3}}$$

$$\therefore A_i = -109.99 \approx -110 \text{ Any}$$

$$iii) A_v = A_i \times \frac{Z_L}{Z_{in}} = \frac{-110 \times \frac{4.7 \times 10^3}{1505.48}}{1}$$

$$= \frac{-110 \times 4.7 \times 10^3}{1505.48}$$

$$= -343.41 \text{ Any}$$

$$iv) Z_o = \frac{1}{Y_o}$$

we know,

$$Y_o = h_{oe} - \frac{h_{fe} \times h_{re}}{h_{ie} + Z_s} = h_{oe} - \frac{h_{fe} \times h_{re}}{h_{ie} + (R_s || R_1)}$$

$$= 20 \times 10^{-6} - \frac{110 \times 20 \times 10^{-4}}{1600 + (1000 / 4700)}$$

$$= 20 \times 10^{-6} - \frac{110 \times 2 \times 10^{-4}}{1600 + \frac{1000 \times 4700}{1000 + 4700}}$$

$$\therefore Y_o = 1.153 \times 10^{-5} \text{ A/V}$$

Now,

$$Z_o = \frac{1}{Y_o} = \frac{1}{1.153 \times 10^{-5}} = 86.71 \text{ k}\Omega$$

Also,

$$Z_{o'} = Z_o || Z_L = \frac{86.71 \times 4.7 \times 10^3}{86.71 + 4.7 \times 10^3}$$


$$= \frac{86.71 \times 4.7 \times 10^3}{86.71 + 4.7 \times 10^3}$$

$$= 4.45 \text{ k}\Omega \text{ Any}$$


## Multistage amplifier (Prabin chaudhary)

2019-Spring

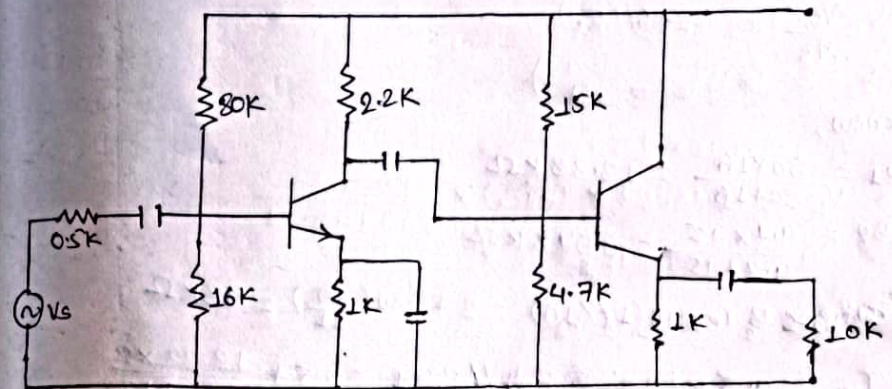4.b. find  $V_L/V_s$  in the circuit below. ( $\beta_1 = \beta_2 = 100$ ,  $r_{e1} = r_{e2} = 20 \Omega$ )  
 The given circuit is:



The re-model of given circuit is:

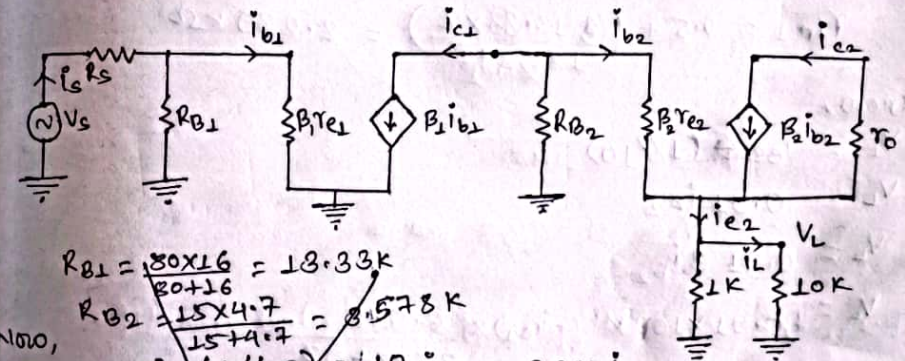

$$R_{B1} = \frac{80 \times 16}{80 + 16} = 13.33 \text{ k}\Omega$$

$$R_{B2} = \frac{15 \times 4.7}{15 + 4.7} = 3.578 \text{ k}\Omega$$

Now,

$$V_L = i_{e2} (1 || 10) = \frac{10}{11} i_{e2} = 0.91 i_{e2}$$

$$\Rightarrow V_L = 0.91 i_{e2} = \beta i_{b2} (0.91)$$

$$\Rightarrow V_L = 100 \times 0.91 i_{b2}$$

$$\Rightarrow V_L = 91 \times \frac{R_{B2}}{\beta r_{e2} \times R_{B2}} \times (-i_{c1})$$

$$\Rightarrow V_L = -91 i_{c1} \times \frac{3.578 \times 1000}{100 \times 20 + 3.578 \times 100} = -58.87 i_{c1}$$



$$\Rightarrow V_L = -58.37 i_{c1}$$

$$\Rightarrow V_L = -58.37 \times \beta_1 i_{b1}$$

$$\Rightarrow V_L = -58.37 \times 100 \times i_s \times \frac{13.33 \times 1000}{13.33 \times 1000 + 2000}$$

$$\Rightarrow V_L = -7678.38 i_s$$

$$\Rightarrow V_L = -7678.38 \times \frac{V_s}{R_{in}}$$

$$\Rightarrow \frac{V_s}{R_{in}} = -76$$

We know,

$$R_{B1} = \frac{80 \times 16}{80 + 16} = 13.33 \text{ K}\Omega$$

$$R_{B2} = \frac{4.7 \times 15}{4.7 + 15} = 3.578 \text{ K}\Omega$$

$$R_{B2} = \beta_2 r_{e2} + R_2 (1/\beta_2) = 2 + 100 \left( \frac{10}{11} \right) = 93 \text{ K}\Omega$$

$$R_{in1} = 0.5 + \left( \frac{13.33 \times 2}{13.33 + 2} \right) = 2.239 \text{ K}\Omega$$

$$R_{B1} = \beta_1 r_{e2} = 2 \text{ K}\Omega$$

$$R_{in1} = 0.5 + \left( \frac{13.33 \times 2}{13.33 + 2} \right) = 2.239 \text{ K}\Omega$$

We know,

$$V_L = i_{e2} (1/\beta_2)$$

$$\Rightarrow V_L = 0.91 i_{e2}$$

$$\Rightarrow V_L = 0.91 \beta_1 i_{b2}$$

$$\Rightarrow V_L = 0.91 \times 100 \times (-i_{c1}) \times \frac{3.578}{3.578 + 93}$$

$$\Rightarrow V_L = -3.371 i_{c1}$$

$$\Rightarrow V_L = -3.371 \times \beta_1 i_{b1}$$

$$\Rightarrow V_L = -3.371 \times 100 \times i_{b1}$$

$$\Rightarrow V_L = -337.1 \times \frac{V_s}{R_{in1}} \times \frac{13.33}{13.33 + 2}$$

$$\Rightarrow V_L = -293.1 V_s$$


$$\Rightarrow V_L = -293.1 \times \frac{V_s}{R_{in1}}$$

$$\Rightarrow \frac{V_L}{V_s} = \frac{-293.1}{2.239} = -130.9$$


2015-Spring

Q. Find the overall voltage gain of cascaded transistor amplifier as shown in figure below. (Given  $r_{e1} = r_{e2} = 25 \Omega$  and  $\beta_1 = \beta_2 = 110$ ).

The given cascaded amplifier is:

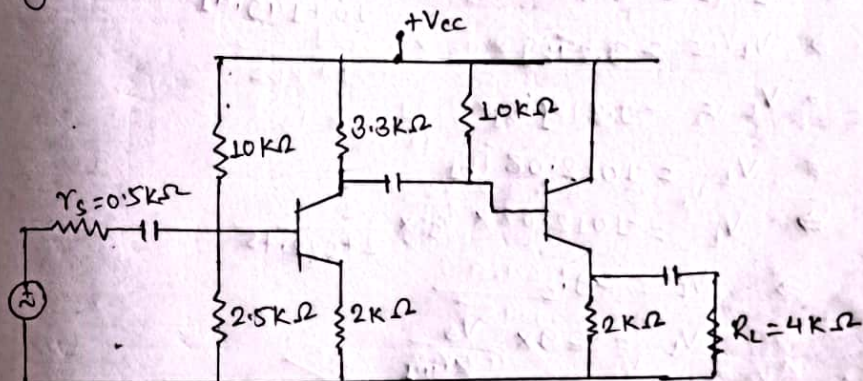

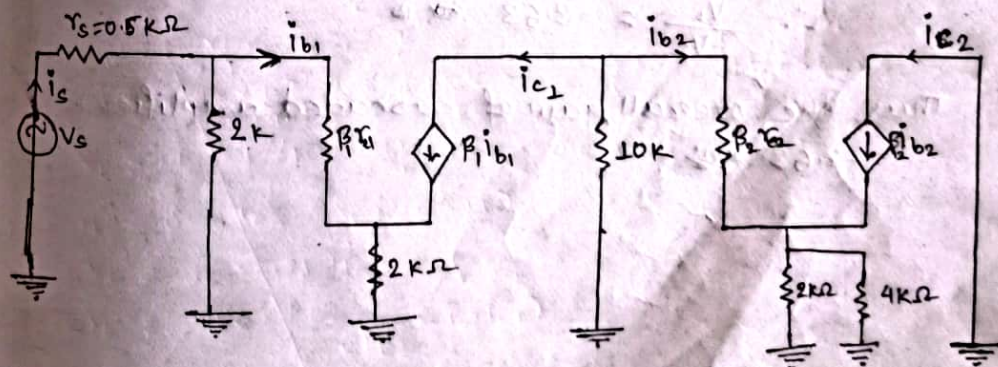The  $r_{e2}$  model of given cascaded amplifier is:







$$R_{b2} = \beta_2 (r_{e2} + R_E // R_L) = 110 \left( 25 \times 10^{-3} + \frac{2 \times 4}{2+4} \right) = 149.41 \text{ K}\Omega$$

$$R_{b1} = \beta_1 (r_{e1} + R_{E1}) = 110 \left( 25 \times 10^{-3} + 2 \right) = 222.75 \text{ K}\Omega$$

$$r_{in1} = r_s + 0.5 + \left( \frac{2 \times 222.75}{2 + 222.75} \right) = 2.48 \text{ K}\Omega$$

we know that,

$$V_L = i_{e2} (R_{E2} // R_L)$$

$$\Rightarrow V_L = \beta_2 i_{b2} \left( \frac{2 \times 4}{2+4} \right)$$

$$\Rightarrow V_L = 110 \times \frac{4}{3} \times i_{b2}$$

$$\Rightarrow V_L = 146.67 \times (-i_{c1}) \times \frac{10}{10 + 149.41}$$

$$\Rightarrow V_L = -9.2 i_{c1}$$

$$\Rightarrow V_L = -9.2 \beta_1 i_{b1}$$

$$\Rightarrow V_L = -1012.08 i_{b1}$$

$$\Rightarrow V_L = -1012.08 \times i_s \times \frac{2}{2 + 222.75}$$

$$\Rightarrow V_L = -9 i_s$$

$$\Rightarrow V_L = -9 \times \frac{V_s}{r_{in1}}$$


$$\Rightarrow \frac{V_L}{V_s} = \frac{-9}{2.48}$$

$$\therefore \frac{V_L}{V_s} = -3.63$$


Thus, the overall gain of cascaded amplifier is  
-3.63

2019- Fall

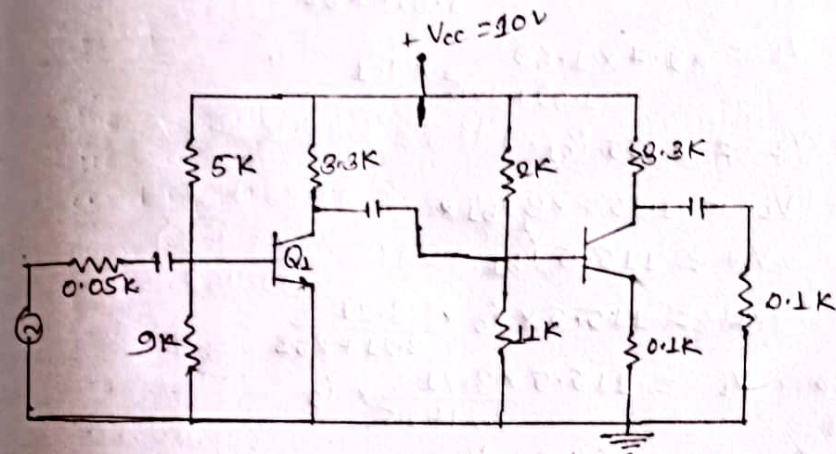4.b. Find  $\frac{V_L}{V_s}$  in the circuit below. ( $\beta_1 = \beta_2 = 100$ ,  $r_{e1} = r_{e2} = 25 \Omega$ )  
The given circuit is.



The re-model of given circuit is:-

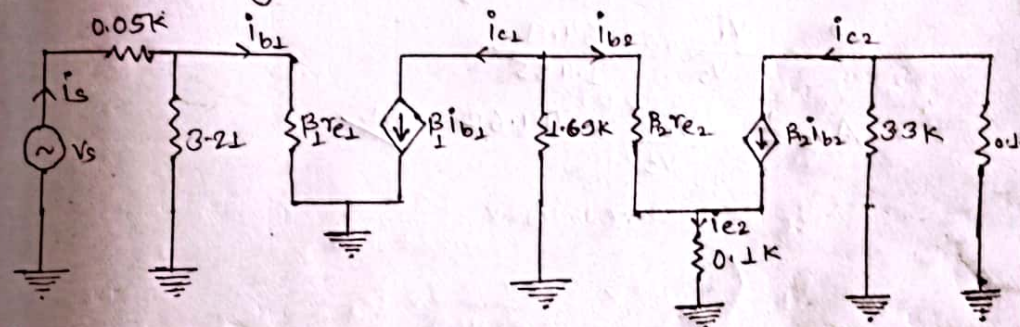

we have,

$$R_{b2} = \beta_2 (r_{e2} + 0.1) = 100 (0.025 + 0.1) = 12.5 \text{ K}\Omega$$

$$R_{b1} = \beta_1 r_{e1} = 100 \times 0.025 = 2.5 \text{ K}\Omega$$

$$r_{in2} = 0.5 + (3.21 // R_{b1}) = 0.5 + \left( \frac{3.21 \times 2.5}{3.21 + 2.5} \right) = 1.455 \text{ K}\Omega$$

we know that,

$$V_L = -i_{c2} \times (3.33 // 0.1)$$

$$\Rightarrow V_L = -i_{c2} \times \frac{3.33 \times 0.1}{3.33 + 0.1}$$

$$\Rightarrow V_L = -0.097 i_{c2}$$



$$\Rightarrow V_L = -0.097 \beta_2 i_{b2}$$

$$\Rightarrow V_L = -0.097 \times 100 i_{b2}$$

$$\Rightarrow V_L = -9.7 i_{b2}$$

$$\Rightarrow V_L = -9.7 \times (i_{c1}) \times \frac{1.69}{1.69 + R_{b2}}$$

$$\Rightarrow V_L = -9.7 \times \frac{1.69}{1.69 + 125} \times i_{c1}$$

$$\Rightarrow V_L = 1.155 i_{c1}$$

$$\Rightarrow V_L = 1.155 \times \beta_1 i_{b1}$$

$$\Rightarrow V_L = 115.5 i_{b1}$$

$$\Rightarrow V_L = 115.5 \times i_s \times \frac{3.21}{3.21 + R_{b2}}$$


$$\Rightarrow V_L = 115.5 \times \frac{3.21}{3.21 + 2.5} \times i_s$$

$$\Rightarrow V_L = 64.9 \times \frac{V_s}{r_{in1}}$$


$$\Rightarrow \frac{V_L}{V_s} = \frac{64.9}{1.455}$$

$$\therefore A_{Vs} = \frac{V_L}{V_s} = 44.62$$

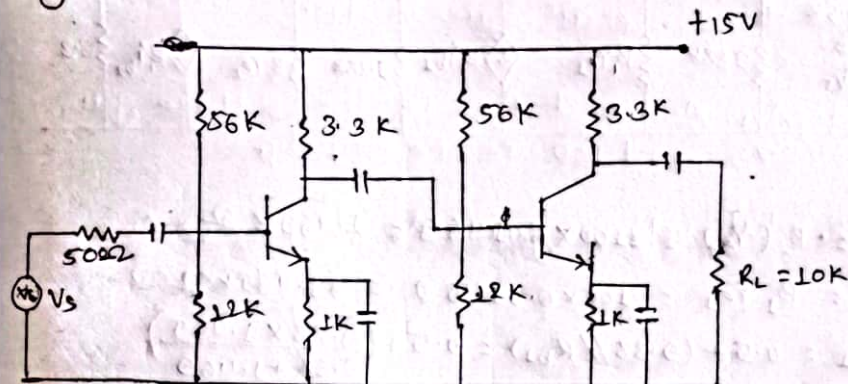Q. For the given 2-stage RC-coupled amplifier circuit, find the overall voltage gain. (Assume  $\beta_1 = \beta_2 = 100$ )  
 Sol. The given circuit is:



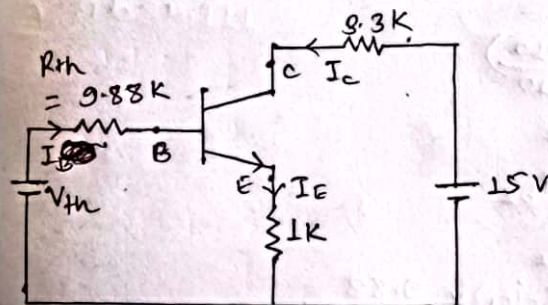The Thevenin's equivalent circuit for stage 1 is:



$$R_{th} = \frac{12 \times 56}{12 + 56}$$

$$\therefore R_{th} = 9.88 \text{ K}$$

$$V_{th} = V_{cc} \times \frac{12}{56 + 12} = 2.647 \text{ V}$$

$\therefore$  Applying KVL in input loop, we get:

$$V_{th} = R_{th} I_B + V_{BE} + I_E R_E$$

$$\Rightarrow 2.647 = 9.88 \times \frac{I_E}{100} + 0.7 + I_E$$

$$\Rightarrow 2.647 - 0.7 = 1.0988 I_E$$

$$\Rightarrow \frac{1.947}{1.0988} = I_E$$


$$\therefore I_E = 1.77 \text{ mA}$$

Now,

$$r_c = \frac{26 \text{ mV}}{1.77 \text{ mA}} = 14.69 \Omega = 0.01469 \text{ K}\Omega$$



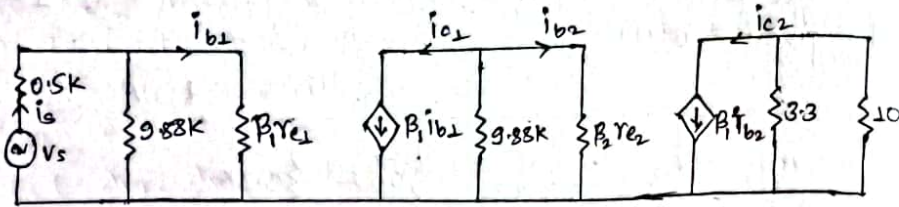The re-model of given RC coupled amplifier is:



Now,

$$R_{b2} = R_2 \parallel r_{e2} = 100 \times 0.01469 = 1.469 \text{ k}\Omega$$

$$R_{b1} = R_1 \parallel r_{e1} = 100 \times 0.01469 = 1.469 \text{ k}\Omega$$

$$r_{in1} = 0.5 + (9.88 \parallel R_{b1}) = 0.5 + \left( \frac{9.88 \times 1.469}{9.88 + 1.469} \right) = 1.778 \text{ k}\Omega$$

We know,

$$V_L = -i_{c2} (3.3 \parallel 10)$$

$$\Rightarrow V_L = -i_{c2} \left( \frac{3.3 \times 10}{3.3 + 10} \right)$$

$$\Rightarrow V_L = -2.48 i_{c2}$$

$$\Rightarrow V_L = -2.48 \beta i_{b2}$$

$$\Rightarrow 2V_L = -248 i_{b2}$$

$$\Rightarrow V_L = -248 \times (-i_{c1}) \times \frac{9.88}{9.88 + R_{b1}}$$

$$\Rightarrow V_L = 248 \times \frac{9.88}{9.88 + 1.469} \times i_{c1}$$

$$\Rightarrow V_L = 215.89 \times \beta i_{b1}$$

$$\Rightarrow V_L = 215.89 \times 100 \times i_{b1}$$

$$\Rightarrow V_L = 21589 i_{b1}$$

$$\Rightarrow V_L = 21589 \times i_s \times \frac{9.88}{9.88 + R_{b1}}$$

$$\Rightarrow V_L = 21589 \times \frac{9.88}{9.88 + 1.469} \times i_s$$

$$\Rightarrow V_L = 18794 \times \frac{V_s}{R_{in1}}$$

$$\Rightarrow V_L = \frac{18794}{1.778} \times V_s$$

$$\Rightarrow \frac{V_L}{V_s} = 10570$$

Q. A 3-stage amplifier has a 1st stage voltage gain of 100, 2nd stage voltage gain of 200 and 3rd stage voltage gain of 400. Find total voltage gain in dB.

sol, Given,

1st stage voltage gain,  $A_{v1} = 100$

2nd stage voltage gain,  $A_{v2} = 200$

3rd stage voltage gain,  $A_{v3} = 400$

Now, The total voltage gain is  $A_v = A_{v1} \times A_{v2} \times A_{v3}$

$$= 100 \times 200 \times 400$$

$$\therefore A_v = 8000000$$

Again,

Total voltage gain in dB,  $A = 20 \log (A_v)$

$$= 20 \log (8 \times 10^6)$$

$$\therefore A_{dB} = 138 \text{ dB}$$

Q. A multistage amplifier employs 5 stages each of which has a power gain of 30. What is the total gain of amplifier in dB?

sol, Given;

Power gain of each stage,  $A_v = 30$

No. of stages,  $N = 5$

$$\therefore \text{Total gain in dB} = N \times 20 \log (A_v)$$

$$= 5 \times 20 \log (30)$$

$$= 29.54 \times 5$$

$$= 147.71 \text{ dB}$$



## Pre-Board :

Q. A 3-stage amplifier has voltage gain of 50, 75 and 100 for the first, second and third stage. Find overall gain in dB.

sol Given:

Let  $A_{v1}$ ,  $A_{v2}$  and  $A_{v3}$  be the voltage gain of 50, 75 and 100 respectively.

$$\begin{aligned} \text{Total voltage gain, } A_v &= A_{v1} \times A_{v2} \times A_{v3} \\ &= 50 \times 75 \times 100 \\ &= 375000 \end{aligned}$$

$$\begin{aligned} \therefore \text{Total voltage gain, } A_v(\text{dB}) &= 20 \log(A_v) \\ &= 20 \log(375000) \\ &= 111.48 \text{ dB} \end{aligned}$$


## Field Effect Transistor (Prabin kushmi)

1. In JFET shown in figure, has transconductance  $4000 \mu\text{S}$  at its bias point. Its drain resistance is  $100 \text{ K}\Omega$ . Assuming small signal model, find the overall voltage gain.


sol Given:

transconductance,  $g_m = 4000 \mu\text{S} = 4 \text{ mS}$   
drain resistance,  $r_d = 100 \text{ K}\Omega$

The given JFET is:

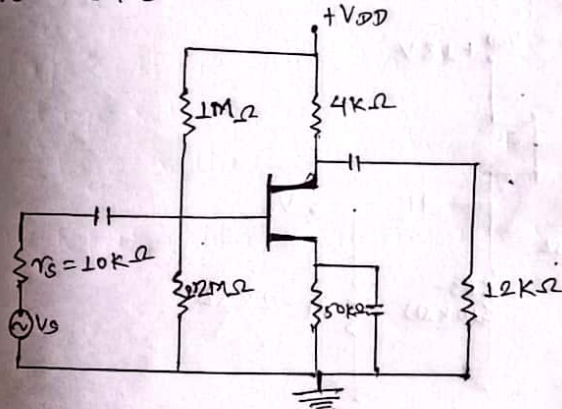

The small signal model of JFET is:

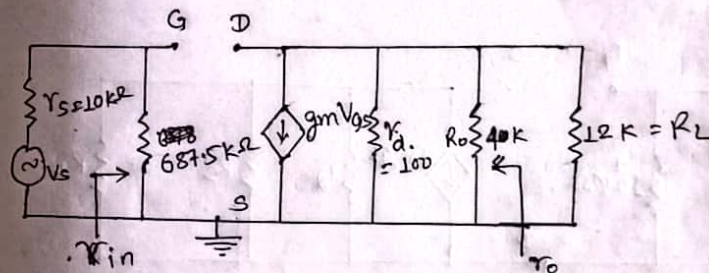

Here,

$$R_{in} = 687.5 \text{ K}\Omega$$

$$R_o = r_d // R_o = \frac{100 \times 4}{100 + 4} = 3.846 \text{ K}\Omega$$

$$A_v = -g_m R_o = -4 \times 10^{-3} \times 3.846 \times 1000 = -15.384$$

$$\begin{aligned} A_{vs} = \frac{V_L}{V_s} &= A_v \times \left( \frac{R_{in}}{r_s + R_{in}} \right) \times \left( \frac{R_L}{R_L + R_o} \right) \\ &= -15.384 \times \left( \frac{687.5}{10 + 687.5} \right) \times \left( \frac{12}{12 + 3.846} \right) = -11.48 \end{aligned}$$



2. Calculate  $Z_{in}$ ,  $Z_o$ ,  $A_v$  for the common drain JFET shown in figure. Given  $I_{DSS} = 10\text{mA}$ ,  $V_p = -5\text{V}$ ,  $r_d = 100\text{k}\Omega$ .


sol Given:

$$I_{DSS} = 10\text{mA} = 10 \times 10^{-3}\text{A}$$


$$V_p = -5\text{V}$$

$$r_d = 100\text{k}\Omega$$

The given JFET is:

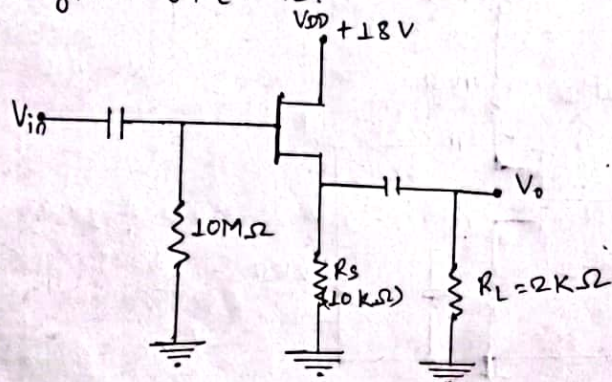

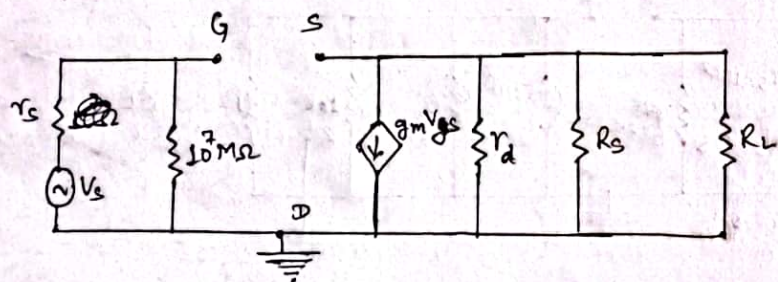The small signal model of given figure is



$$g_m = \frac{-2 I_{DSS}}{V_p} \left( 1 - \frac{V_{GS}}{V_p} \right)$$

$$\therefore V_{GS} \mid V_p = -0.7 = -5 - 0.7 = -4.3$$

$$\therefore V_{GS} = -4.3$$

$$\text{Now, } g_m = \frac{-2 \times 10^{-2}}{-5} \left( 1 - \frac{-4.3}{-5} \right) = 4 \times 10^{-3} \times 0.14 = 0.56 \text{ ms}$$

$$r_o = R_s \parallel r_d + \frac{1}{g_m} = \frac{10 \times 100}{10 + 100} + \frac{1}{0.56 \text{ ms}}$$


$$\therefore r_o = 10.876 \text{ k}\Omega$$

$$\begin{aligned} \text{Now, voltage gain, } A_v &= \frac{V_o}{V_{in}} = \frac{g_m V_{GS} (r_d \parallel R_s)}{V_{GS} + g_m V_{GS} (R_s \parallel r_d)} \\ &= \frac{g_m (r_d \parallel R_s)}{1 + g_m (R_s \parallel r_d)} \\ &= \frac{0.56 \times (20 \parallel 100)}{1 + 0.56 \times (20 \parallel 100)} \\ &= \frac{0.56 \times 16.67}{1 + 0.56 \times 16.67} \\ \therefore A_v &= 0.9 \text{ Ans} \end{aligned}$$

2015 - Fall

4.b. Determine  $I_{DQ}$  and  $V_{DSQ}$  for the given below. Given  $I_{DSS} = 8\text{mA}$  and  $V_p = -8\text{V}$ .

sol The given circuit is:

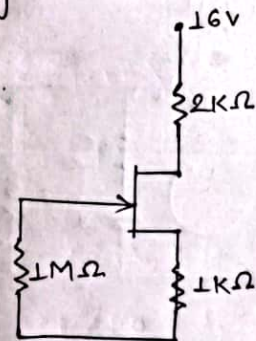





## DC power Supply (Prabin Chaudhary)

### Clamper Circuit:

1. Draw output waveform of given circuit. (Assume ideal diode).

2. The given circuit is:

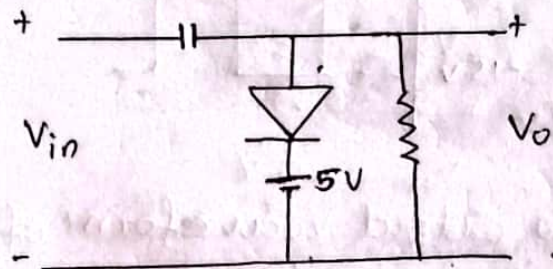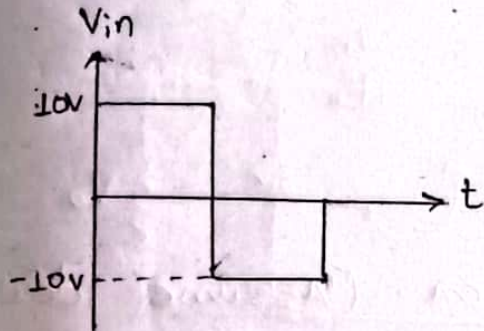

Here

i) For positive half cycle


→ Replace the diode by short circuit.

Applying KVL in input loop,

we get:  $V_{in} - V_c - 5 = 0$

→  $10 - 5 = V_c$

∴  $V_c = 5V$

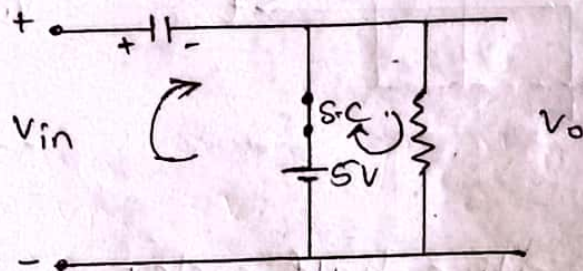

Applying KVL in output loop, we get:

$5 - V_o = 0$

$V_o = 5V$

ii) For negative half cycle.

→ Replace the diode by open circuit.


Applying KVL in loop, we get:

$-V_{in} - V_c - V_o = 0$

→  $-V_o = V_{in} + V_c$


→  $-V_o = 10 + 5$

∴  $V_o = -15V$

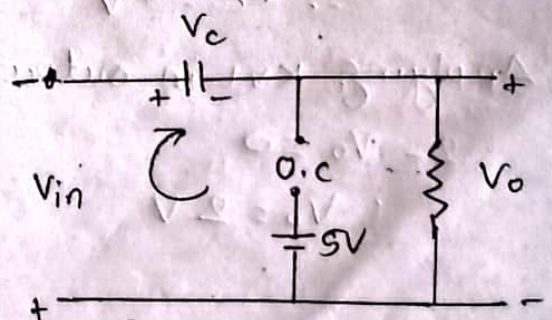





The output waveform is:

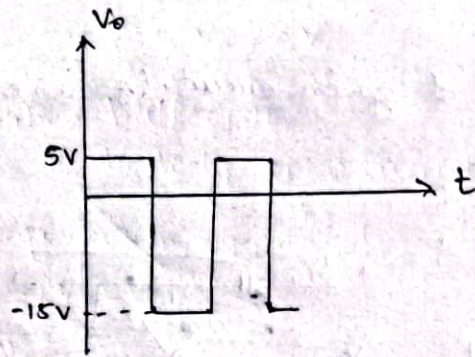

2. Draw output waveform of given. (Assume ideal diode).

so The given circuit is:

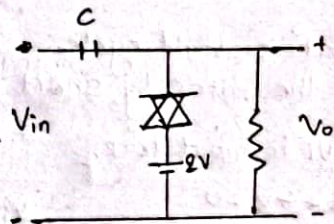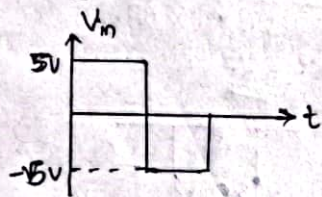

i) For positive half cycle.

⇒ Replace the diode by short circuit.

Applying KVL in input loop,

$$V_{in} + 2 - V_c = 0$$

$$\Rightarrow V_{in} + 2 - V_c = 0$$


$$\Rightarrow 5 + 2 - V_c = 0$$

$$\therefore V_c = 7V$$

Applying KVL in output loop,

$$2 - V_o = 0$$

$$\therefore V_o = 2V$$

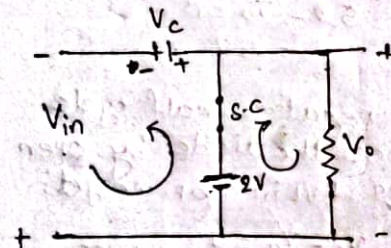

ii) For negative half cycle  
⇒ Replace the diode by open circuit.


Applying KVL in loop, we get:

$$V_{in} + V_c - V_o = 0$$


$$\Rightarrow V_{in} + V_c = V_o$$

$$\Rightarrow V_o = 5 + 7$$

$$\therefore V_o = 12V$$


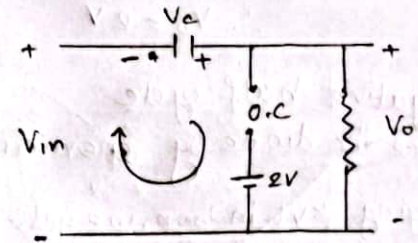


The output waveform is:

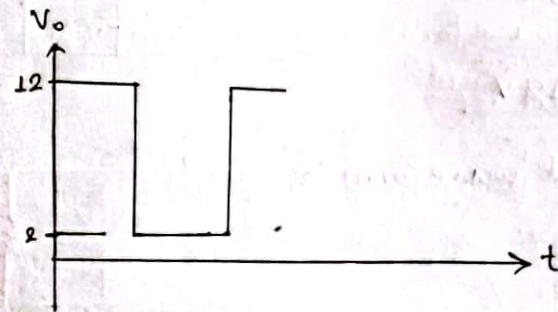

3. Draw the output waveform of given circuit. (Assume Si diode)

so The given circuit is:

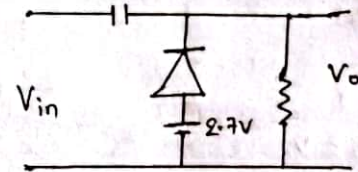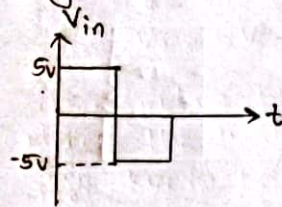

i) For positive half cycle.


⇒ Replace the diode by short circuit, 0.7V (Si diode).

Applying KVL in input loop, we get:

$$V_{in} + 2.7 - 0.7 - V_c = 0$$

$$\Rightarrow 5 + 2 = V_c$$

$$\therefore V_c = 7V$$

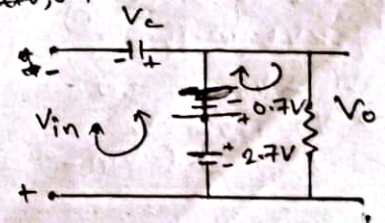



Applying KVL in output loop, we get:

$$2.7 - 0.7 - V_o = 0$$

$$\therefore V_o = 2V$$

ii) For negative half cycle

→ Replace the diode by open circuit.

Applying KVL in loop, we get:

$$V_{in} + V_c - V_o = 0$$



$$\Rightarrow V_{in} + 7 - 0 = 0$$

$$\therefore V_{in} = -7V$$


$$\Rightarrow 5 + 7 = V_o$$

$$\therefore V_o = 12V$$

The given output waveform is:

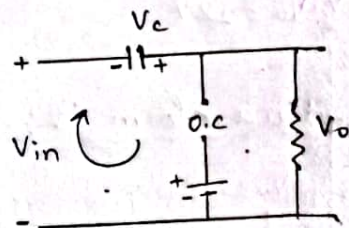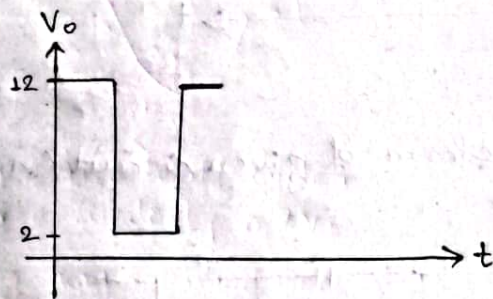

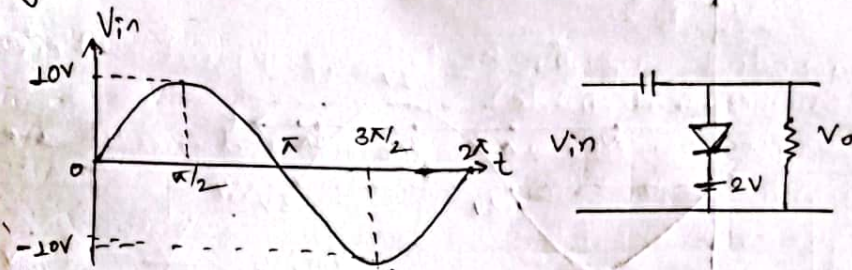4. Draw output waveform. (Assume ideal diode).  
 Sol. The given circuit is:




i) For positive half cycle of input:  
 → Replace the diode by short circuit

Apply KVL in input loop, we get,

$$V_{in} - V_c - 2 = 0$$

$$\Rightarrow V_c = V_{in} - 2$$

$$\Rightarrow V_o = 10 - 2 = 8$$

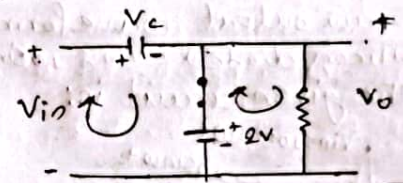

Apply KVL in output loop, we get:

$$2 - V_o = 0$$

$$\therefore V_o = 2$$

ii) For negative half cycle of input:


→ Replace the diode by open circuit

Apply KVL in the loop, we get:

$$V_{in} + V_c + V_o = 0$$

$$\Rightarrow V_{in} + 8 + V_o = 0$$

$$\therefore V_o = -V_{in} - 8$$

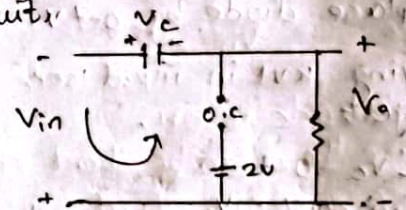


Now

| wt       | 0  | $\pi/2$ | $\pi$ | $3\pi/2$ | $2\pi$ |
|----------|----|---------|-------|----------|--------|
| $V_{in}$ | 0  | 10      | 0     | -10      | 0      |
| $V_o$    | -8 | 8       | -8    | 2        | -8     |





Thus the output waveform will be.

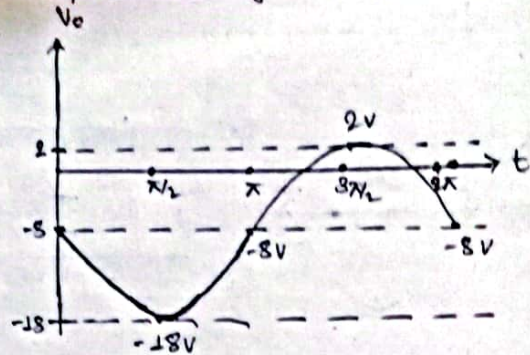

5. Draw output waveform of given circuit. (Assume Silicon diode),  $V_{in} = 10 \sin \omega t$ .

The given circuit is:

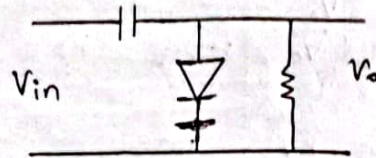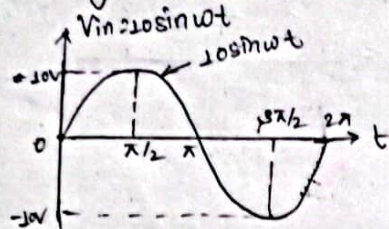

i) For positive half cycle:


→ Replace diode by 0.7V.

Applying KVL in input loop, we get;

$$V_{in} - V_c - 0.7 = 0$$

$$\Rightarrow 10 - 0.7 = V_c$$

$$\therefore V_c = 9.3V$$

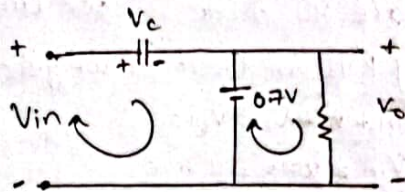

ii) For negative half cycle:


→ Replace the diode by Open circuit:

Apply KVL in the loop, we get;

$$V_{in} + V_o + V_c = 0$$

$$\Rightarrow V_o = -V_{in} - V_c$$


$$\Rightarrow V_o = -(-10) - 9.3V$$

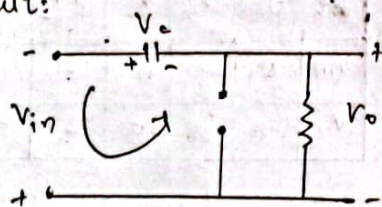

| $\omega t$ | 0    | $\pi/2$ | $\pi$ | $3\pi/2$ | $2\pi$ |
|------------|------|---------|-------|----------|--------|
| $V_{in}$   | 0    | 10      | 0     | -10      | 0      |
| $V_o$      | -9.3 | 2       | -9.3  | 2        | -9.3   |

$$V_o = -V_{in} - 9.3$$

The output waveform will be


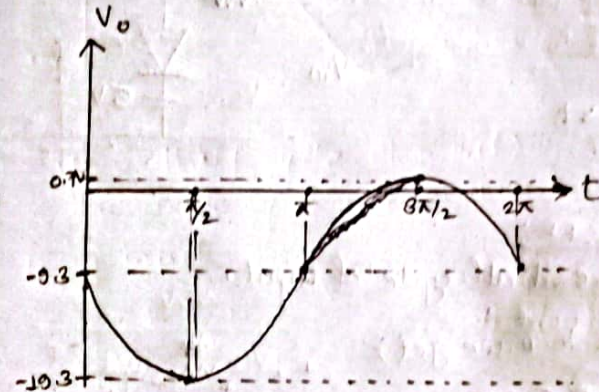




## Clipping Circuits (Prabin Chaudhary)

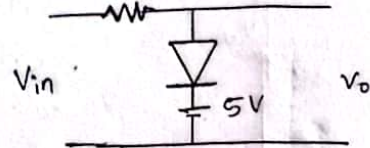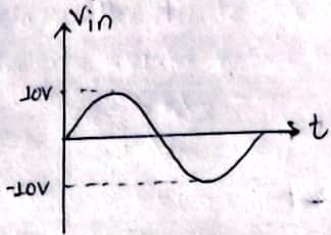1. Draw output waveform for following input and circuit.  
(Assume ideal diode)

sq The given input and waveform and circuit are:



consider a positive half cycle of input.

Applying KVL in the loop, we get:

$$V_{in} - V_D - 5 = 0$$

$$\Rightarrow V_{in} - 5 = V_D$$


$$\therefore V_D = V_{in} - 5$$

Condition for diode to be ON.

$$V_D > 0$$

$$\Rightarrow V_{in} - 5 > 0$$

$$\therefore V_{in} > 5V$$

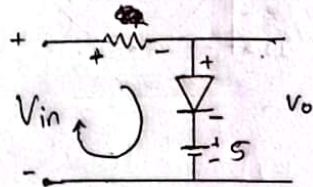


1) If the diode is ON.

⇒ Replace the diode by short circuit.

Applying KVL in output loop,

$$5 - V_o = 0$$

$$\therefore V_o = 5V$$

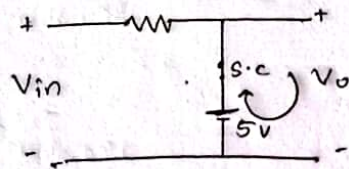


2) If the diode is OFF,  
⇒ Replace the diode by open circuit.

Applying KVL in output loop,

$$V_{in} - V_o = 0$$

$$\therefore V_o = V_{in}$$

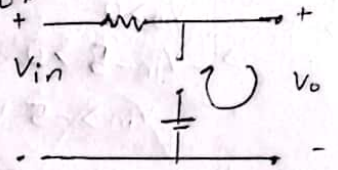


Now,

Condition is,  $V_{in} > 5$

Diode ON,  $V_o = 5V$



Diode OFF,  $V_o = V_{in}$

Thus the output waveform will be

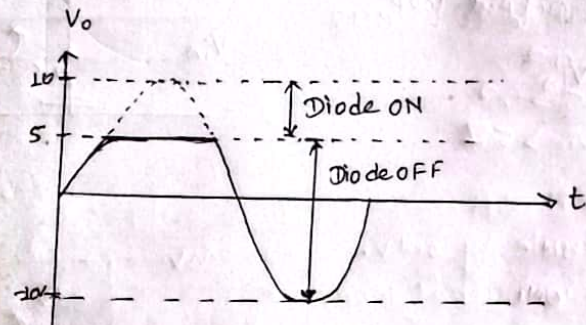

2. Draw output waveform of given input waveform and circuit. (Assume ideal diode)

sq The given waveform and circuit is:

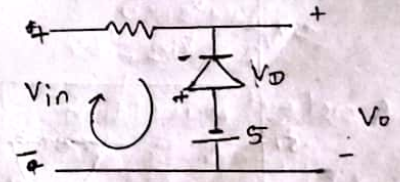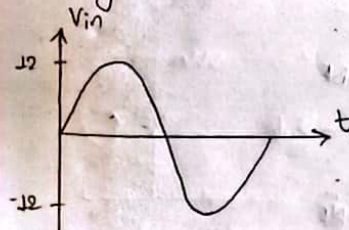

Applying KVL in input loop, we get:-

$$V_{in} + V_D + 5 = 0$$

$$\Rightarrow V_D = -V_{in} - 5$$



Condition for diode to be ON,

$$V_D > 0$$

$$\Rightarrow -V_{in} - 5 > 0$$

$$\Rightarrow V_{in} > -5V \Rightarrow V_{in} > -5V$$


If the diode is ON:

→ Replace the diode by open circuit.

Applying KVL in input loop, we get:

$$-5 + V_D = 0$$

$$\therefore V_D = 5V$$

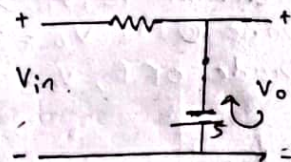


If the diode is OFF:

→ Replace the diode by short circuit.

Applying KVL in output loop,

$$V_{in} - V_D = 0$$

$$\therefore V_D = V_{in}$$

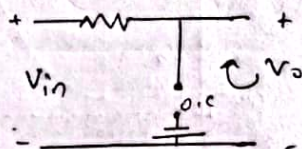


Condition is,

$$V_{in} \geq 5V$$



$$V_D = -5V \text{ For ON}$$

$$V_D = V_{in} \text{ For OFF}$$

The output waveform will be

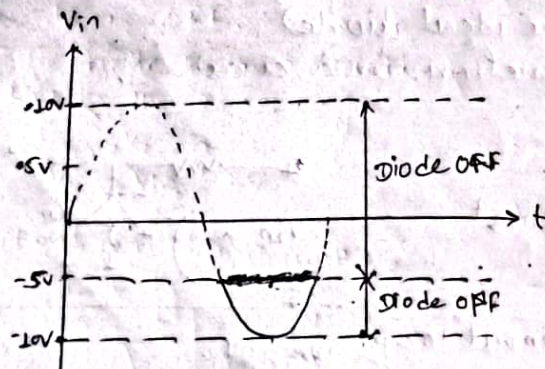

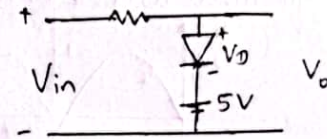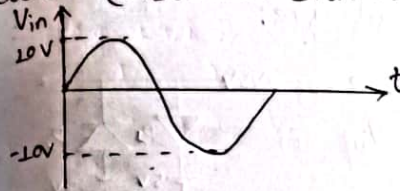3. Draw the output waveform of given input waveform and circuit. (Assume silicon diode)




Consider positive half cycle of input.

Applying KVL in input loop, we get:

$$V_{in} - V_D - 5 = 0$$

$$\therefore V_D = V_{in} - 5$$

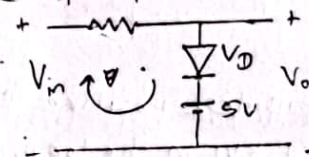

Condition for diode to be ON,

$$V_D > 0.7$$

$$\Rightarrow V_{in} > 0.7$$

$$\therefore V_{in} > 5.7V$$


→ If the diode is ON:

→ Replace the diode by short circuit.

Applying KVL in output loop,

$$5 - V_D = 0.7$$

$$\therefore V_D = 5 - 0.7 = 4.3V$$

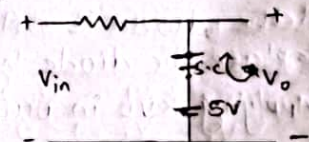


→ If the diode is OFF:

→ Replace the diode by open circuit.


Applying KVL in output loop, we get:

$$V_D = V_{in}$$

$$\therefore V_D = V_{in}$$

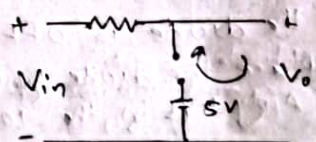



Thus the output waveform will be

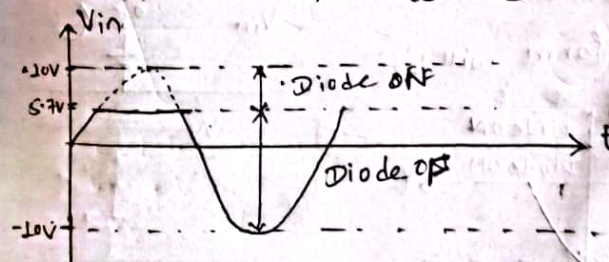



4. Draw output waveform. (Assume silicon diode)

⇒ The input waveform and circuit are:

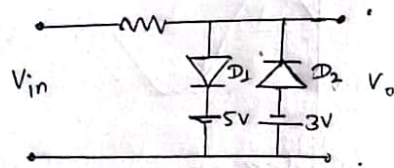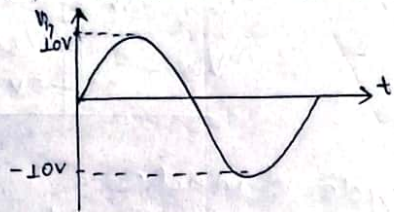

~~Consider~~ Consider positive half cycle of diode  $D_1$  only.

Applying KVL in the loop, we get:

$$V_{in} - V_D - 5V = 0$$


$$\therefore V_D = V_{in} - 5V$$

Condition for diode to be ON,

$$V_D > 0.7$$

$$\Rightarrow V_{in} - 5 > 0.7$$

$$\therefore V_{in} > 5.7$$

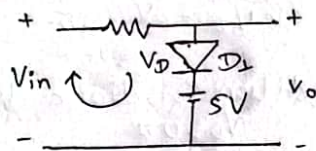


i) If the diode is ON

⇒ Replace the diode by  $0.7V$ .

Applying KVL in Output loop,

$$5 + 0.7 - V_o = 0$$

$$\therefore V_o = 5.7V$$

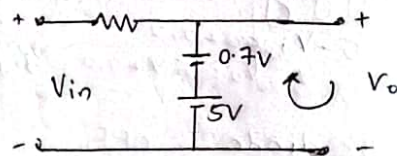


ii) If the diode is OFF.

⇒ Replace the diode by open circuit.


Apply KVL in the loop, we get,

$$V_{in} - V_o = 0$$

$$\therefore V_o = V_{in}$$

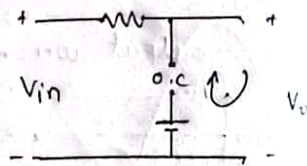

Thus the output waveform will be

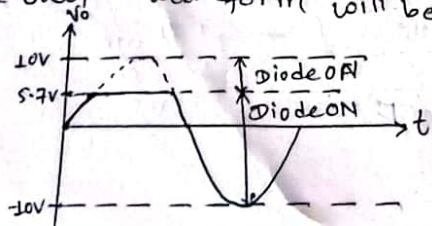

Again Consider ~~positive~~ <sup>negative</sup> half cycle of Diode  $D_2$  only.

Apply KVL in the loop, we get:

$$V_{in} + V_D + 3 = 0$$

$$\Rightarrow V_D = -V_{in} - 3$$


Condition for diode to be ON,

$$V_D > 0.7$$

$$\Rightarrow -V_{in} - 3 > 0.7$$

$$\therefore V_{in} < -3.7$$

$$\therefore V_{in} < -3.7V$$

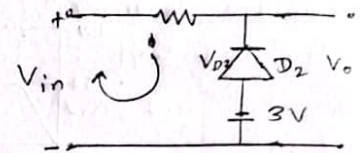


If diode is ON:

Replace the diode by  $0.7V$ .

Applying KVL in output loop, we get:

$$-3 - 0.7 - V_o = 0$$

$$\therefore V_o = -3.7V$$

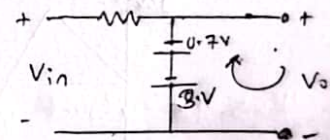


If diode is OFF:

Replace the diode by open circuit.


Applying KVL in the output loop,

$$V_{in} - V_o = 0$$

$$\therefore V_o = V_{in}$$

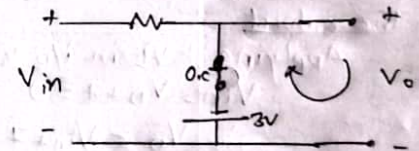


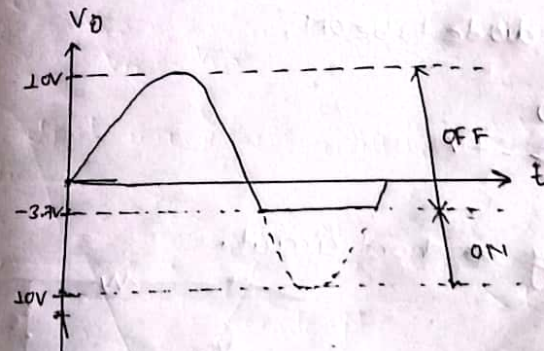So the output waveform for  $D_2$  will be






⊙ Thus the final output waveform will be

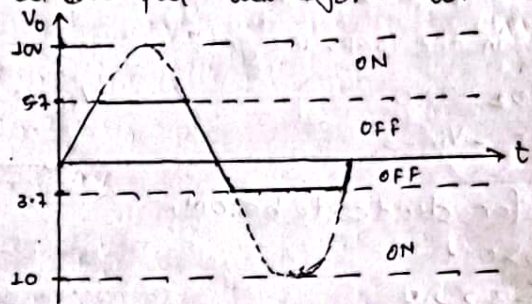

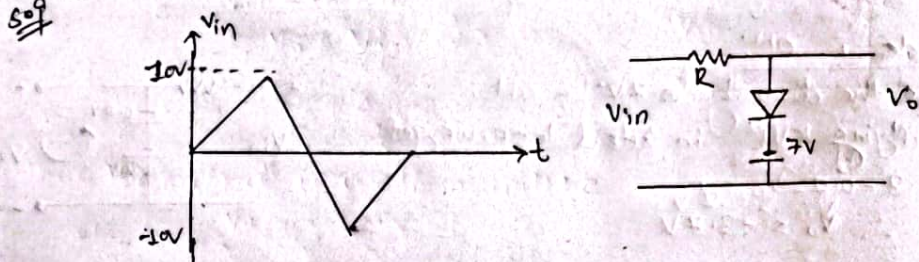5. Draw output waveform. (assume ideal diode)




Consider positive half cycle of diode only

~~The output~~

Applying KVL in i/p loop

$$V_{in} - V_D + 7 = 0$$

$$\therefore V_D = V_{in} + 7$$

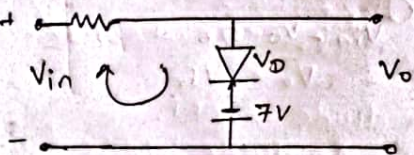

~~If the diode is ON:~~

Condition for diode to be ON,

$$V_D > 0$$

$$\Rightarrow V_{in} + 7 > 0$$


$$\therefore V_{in} > -7V$$

⊙ If the diode is ON

⇒ Replace the diode by short circuit.

$$-7 - V_o = 0$$

$$\therefore V_o = -7V$$

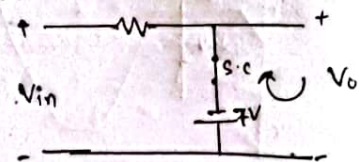


⊙ If the diode is OFF

⇒ Replace the diode by open circuit.


Applying KVL in loop,

$$V_{in} - V_o = 0$$

$$\therefore V_o = V_{in}$$


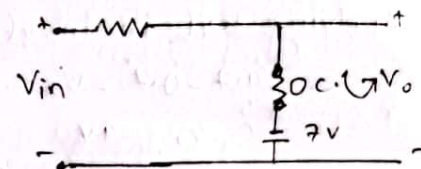


The output waveform will be.

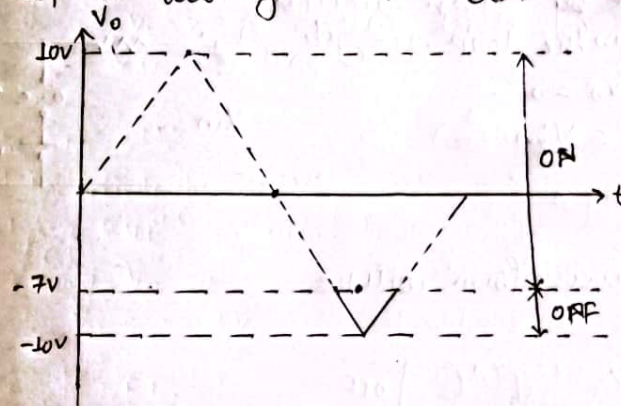

6. Draw output waveform. (Assume practical diode)

⇒

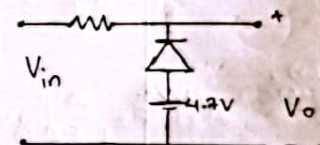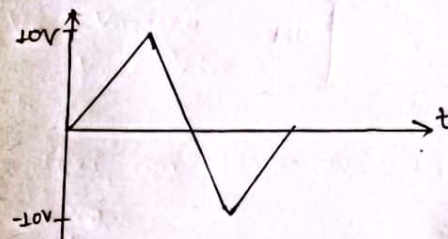

⊙ Consider for positive half cycle of a diode.

Applying KVL in the loop, we get:

$$V_{in} + V_D - 4.7 = 0$$


$$\therefore V_D = -V_{in} + 4.7$$

Condition for diode to be ON,

$$V_D > 0.7$$

$$\Rightarrow -V_{in} + 4.7 > 0.7$$

$$\therefore V_{in} < 4V$$

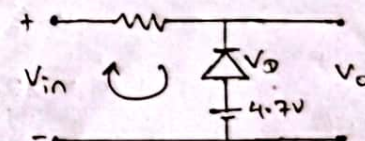




If the diode is ON

→ Replace the diode by 0.7V.

Applying KVL in input loop, we get:

$$4.7 - 0.7 - V_o = 0$$

$$\therefore V_o = 4V$$

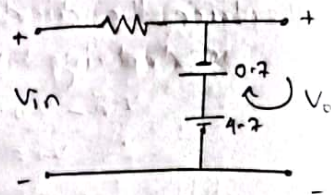


If the diode is OFF:

→ Replace the diode by open circuit.


Applying KVL in the loop, we get:

$$V_{in} - V_o = 0$$

$$\therefore V_o = V_{in}$$

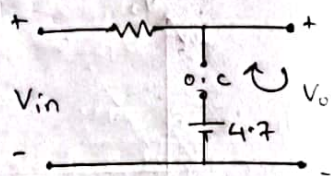

Thus the output waveform will be

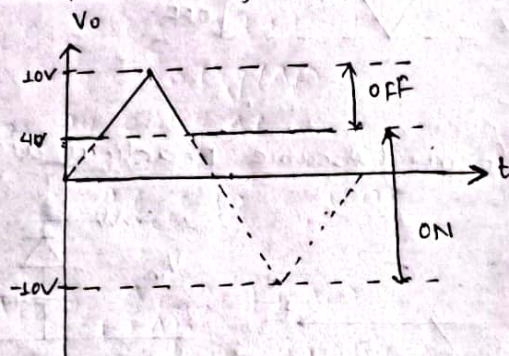

## Feedback Amplifier (Prabin)

1. The voltage gain of an amplifier without feedback is 3000. Calculate the voltage gain of the amplifier if negative feedback is introduced in the circuit. (Given feedback factor = 0.01)

sol Given;

without voltage gain,  $A = 3000$

feedback factor,  $B = 0.01$

voltage gain with feedback,  $A_f = ?$

we know that,

$$A_f = \frac{A}{1 + AB}$$

$$= \frac{3000}{1 + 3000 \times 0.01}$$

$$\therefore A_f = 96.77 \text{ Ans}$$

2. The overall gain of an multistage amplifier is 140. When negative feedback is applied the gain is reduced to 17.5. Find the fraction of the output that is feedback to the input.

sol Given;

gain without feedback,  $A = 140$

gain with feedback,  $A_f = 17.5$

feedback ratio,  $B = ?$

we know that,

$$A_f = \frac{A}{1 + AB}$$

$$\Rightarrow 17.5 = \frac{140}{1 + 140B}$$

$$\Rightarrow 1 + 140B = \frac{140}{17.5}$$

$$\Rightarrow 140B = 8 - 1 = 7$$

$$\therefore B = \frac{7}{140} = \frac{1}{20} = 0.05 \text{ Ans}$$



3. The voltage gain of an amplifier without feedback is 60 dB. It decreases to 40 dB with feedback. Calculate the % of output which is feed back to the input.

Sol Given;

~~feedback without~~  
In dB, voltage gain without feedback,  $A = 60 \text{ dB}$   
voltage gain with feedback,  $A_f = 40 \text{ dB}$   
feedback ratio,  $\beta = ?$

we know,

$$60 = 20 \log (A) \Rightarrow$$

$$\Rightarrow \frac{60}{20} = \log A$$

$$\therefore A = 10^3 = 1000$$

Also,

$$40 = 20 \log (A_f)$$

$$\Rightarrow \frac{40}{20} = \log A_f$$

$$\therefore A_f = 10^2 = 100$$

Now,

$$A_f = \frac{A}{1 + A\beta}$$

$$\Rightarrow 100 = \frac{1000}{1 + 1000\beta}$$

$$\Rightarrow 1 + 1000\beta = \frac{1000}{100}$$

$$\Rightarrow 1000\beta = 10 - 1$$

$$\Rightarrow \beta = \frac{9}{1000}$$

$$\therefore \beta = 0.009 \text{ Ans}$$

4. A negative feedback of 0.2% is applied to an amp gain of voltage of 60 dB. Calculate the % change in the overall gain of feedback amplifier if the internal amplifier is subjected to a gain of the reduction of 15%.

Sol Given;

$$\frac{dA_f}{A_f} = 0.2\%$$

$$A_f = 60 \text{ dB}$$

feedback ratio %,  $\beta = 0.2\% = 0.002$

voltage gain in dB with feedback,  $A_f = 60 \text{ dB}$

$$\frac{dA}{A} = 15\%$$

Now,

$$60 = 20 \log (A_f)$$

$$\Rightarrow \frac{60}{20} = \log A_f$$

$$\therefore A_f = 1000$$

Now,

$$\frac{dA_f}{A_f} = \frac{dA}{A} \times \frac{1}{1 + A\beta}$$

$$\Rightarrow \frac{dA_f}{A_f} = \frac{15\%}{1 + 1000 \times 0.002} = 5\%$$

$$\therefore \frac{dA_f}{A_f} = 5\% \text{ Ans}$$



5. An amplifier has the midband gain of 1500 and BW of 4MHz. The midband gain reduces to 150 when a negative feedback is applied. Determine the value of feedback & BW.

Given:

Midband gain,  $A = 1500$

Bandwidth,  $BW = 4\text{MHz}$

Midband gain with feedback,  $A_f = 150$

we know,

$$A_f = \frac{A}{1 + A\beta}$$

$$\Rightarrow \frac{A_f}{A} = \frac{1}{1 + A\beta}$$

$$\Rightarrow \frac{150}{1500} = \frac{1}{1 + 1500\beta}$$

$$\Rightarrow 10 = 1 + 1500\beta$$

$$\Rightarrow \frac{10 - 1}{1500} = \beta$$

$$\therefore \beta = 0.006$$

$\therefore$  feedback ratio,  $\beta = 0.006 = 0.6\%$

Again,

$$BW_f = BW(1 + A\beta)$$

$$= 4 \times 10^6 (1 + 1500 \times 0.006)$$

$$\therefore BW_f = 40\text{MHz}$$